

# NANO-PROCESSOR LAB-REPORT

INDEX NO :- 180048D

PARTNER INDEX NO :- 180711F

## HA

### Tables

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

### Code

entity HA is

Port ( A : in STD\_LOGIC;

B : in STD\_LOGIC;

C : out STD\_LOGIC;

S : out STD\_LOGIC);

end HA;

architecture Behavioral of HA is


begin

S <= A XOR B;


C <= A AND B;

end Behavioral;

### RTL

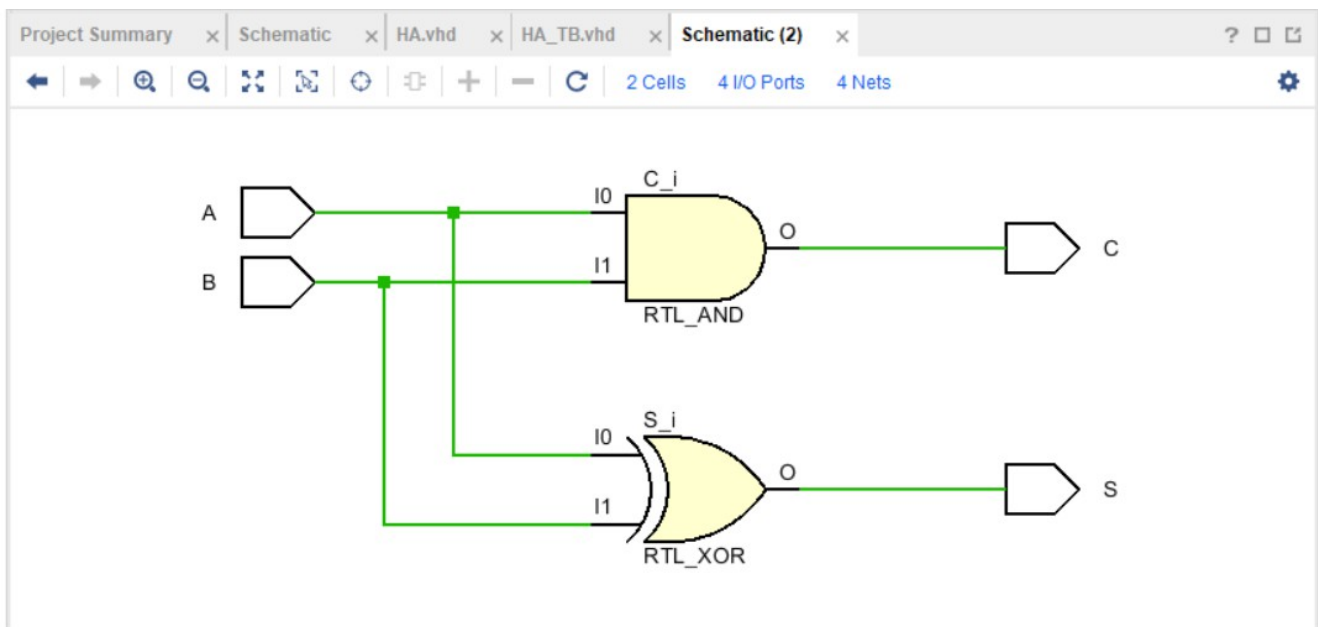

### Synthesized Design

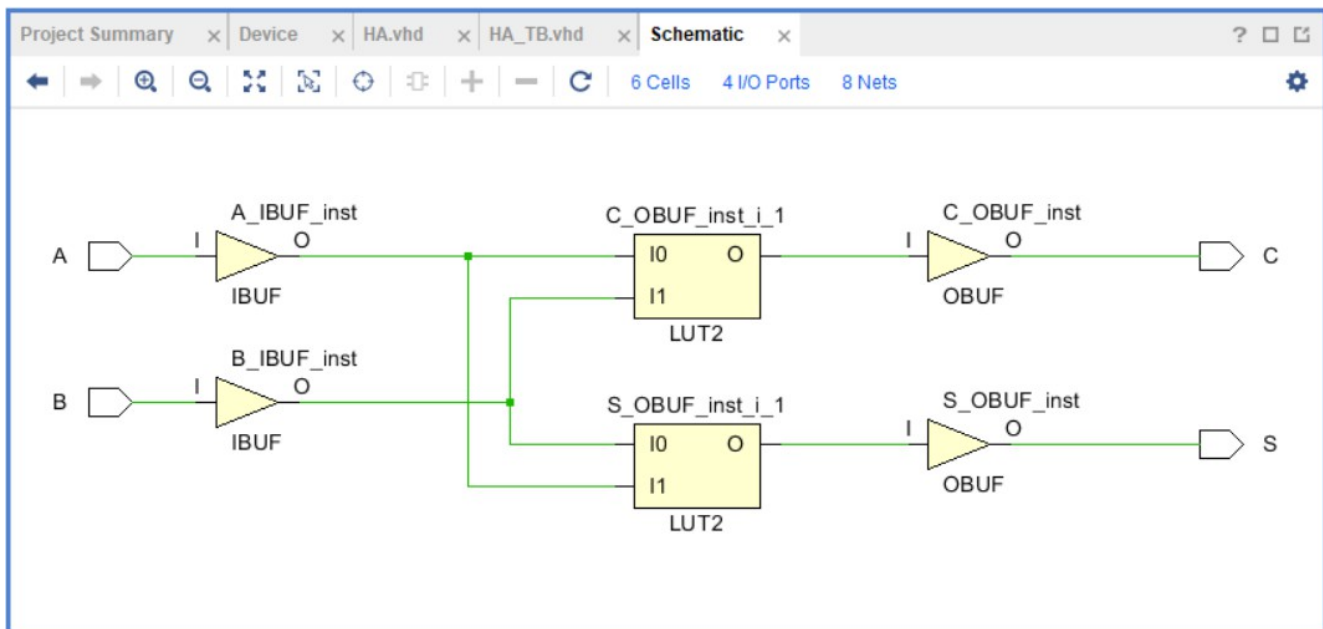

### Simulation Code

entity HA\_TB is

-- Port ();

end HA\_TB;

architecture Behavioral of HA\_TB is

COMPONENT HA

```
Port ( A : in STD_LOGIC;  
      B : in STD_LOGIC;  
      C : out STD_LOGIC;  
      S : out STD_LOGIC);  
END COMPONENT;  
  
SIGNAL A1,B1,C1,S1 :STD_LOGIC;
```

```
begin
```


```
UUT: HA PORT MAP (  
  A => A1,  
  B => B1,  
  S => S1,  
  C => C1);  
SIM: PROCESS  
BEGIN
```

```
  A1 <='0';  
  B1 <='0';  
  WAIT FOR 100 NS;  
  A1 <='0';  
  B1 <='1';  
  WAIT FOR 100 NS;  
  A1 <='1';  
  B1 <='0';  
  WAIT FOR 100 NS;  
  A1 <='1';  
  B1 <='1';  
  WAIT;
```

```
END PROCESS;
```

```
end Behavioral;
```

**Behavioral Simulation**

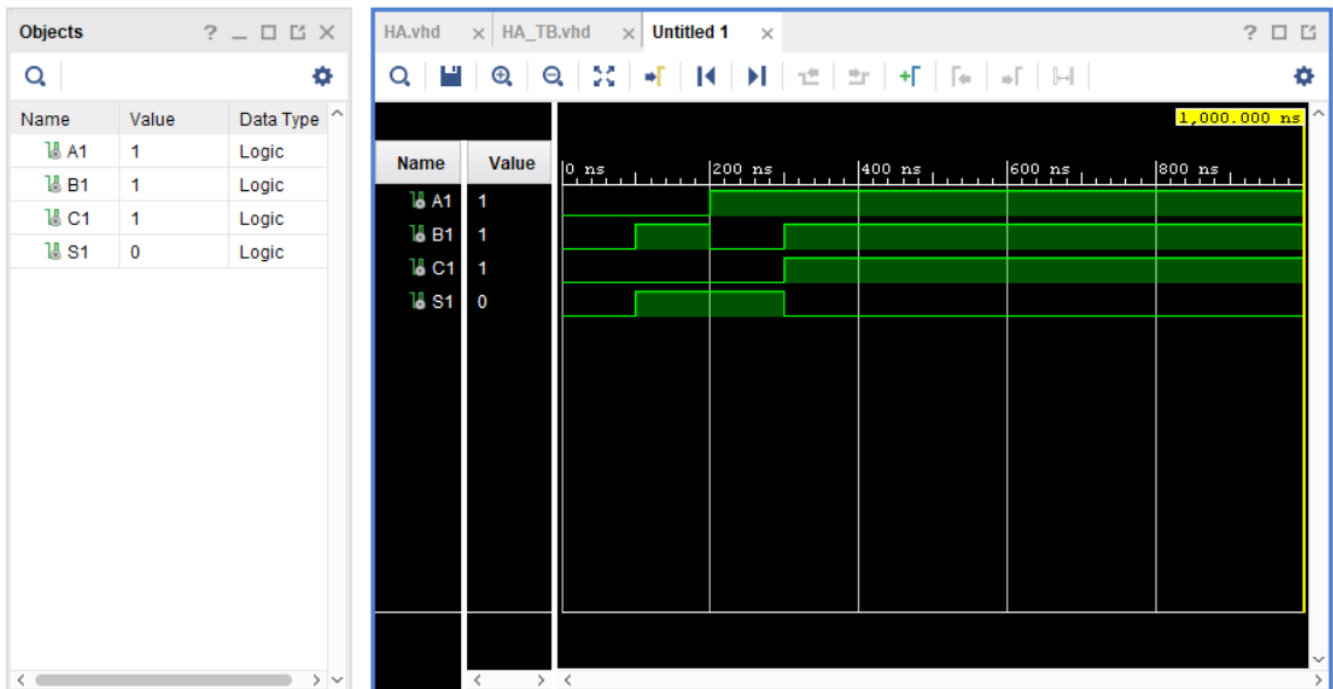

## FA

### Tables

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$S = (A \text{ xor } B) \text{ xor } C_{in}$

$C = (A \text{ and } B) \text{ or } ((A \text{ xor } B) \text{ and } C_{in})$

### Code

entity FA is

```

Port ( A : in STD_LOGIC;
      B : in STD_LOGIC;
      C_in : in STD_LOGIC;
      S : out STD_LOGIC;
      C_out : out STD_LOGIC);

```

end FA;

architecture Behavioral of FA is

component HA

```
Port ( A : in STD_LOGIC;  
      B : in STD_LOGIC;  
      C : out STD_LOGIC;  
      S : out STD_LOGIC);
```

end component;

```
signal ha0_s, ha0_c, hal_c :std_logic;  
begin
```

```
HA0 : HA PORT MAP (
```


```
  A => A,  
  B => B,  
  C => ha0_c,  
  S => ha0_s);
```

```
HA1 : HA PORT MAP (
```


```
  A => ha0_s,  
  B => C_in ,  
  C => hal_c,  
  S => S);
```

```
  c_out <= ha0_c or hal_c;  
end Behavioral;
```

## RTL

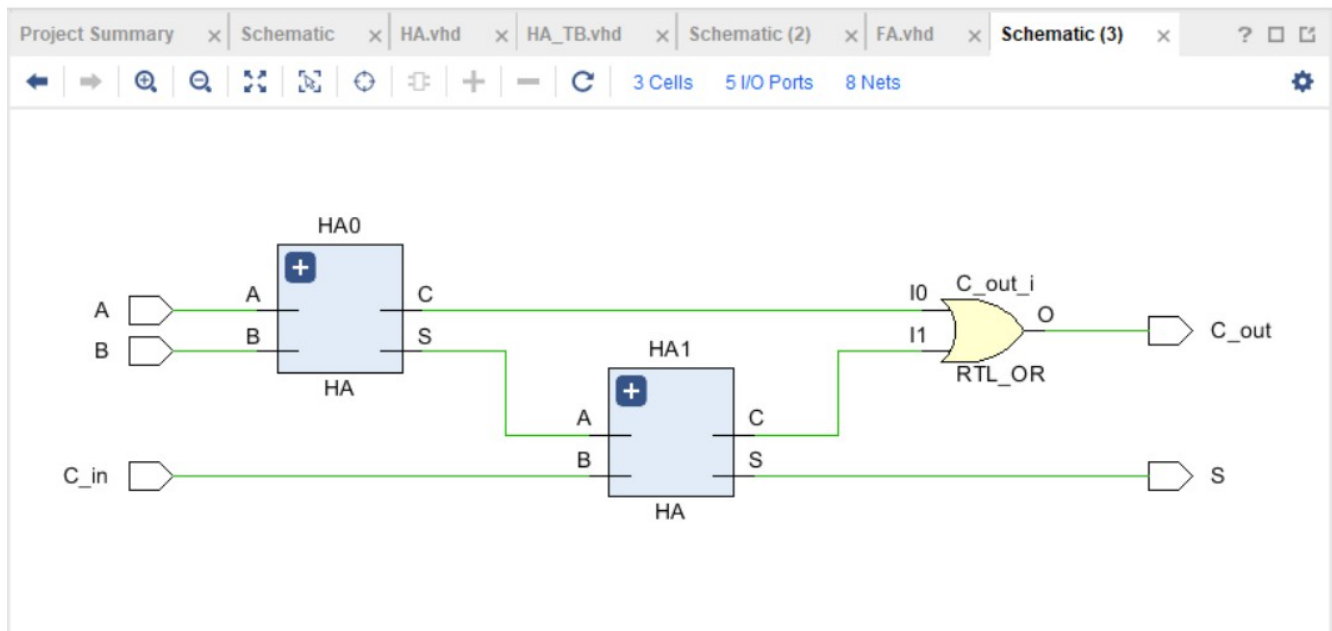

## Synthesized Design

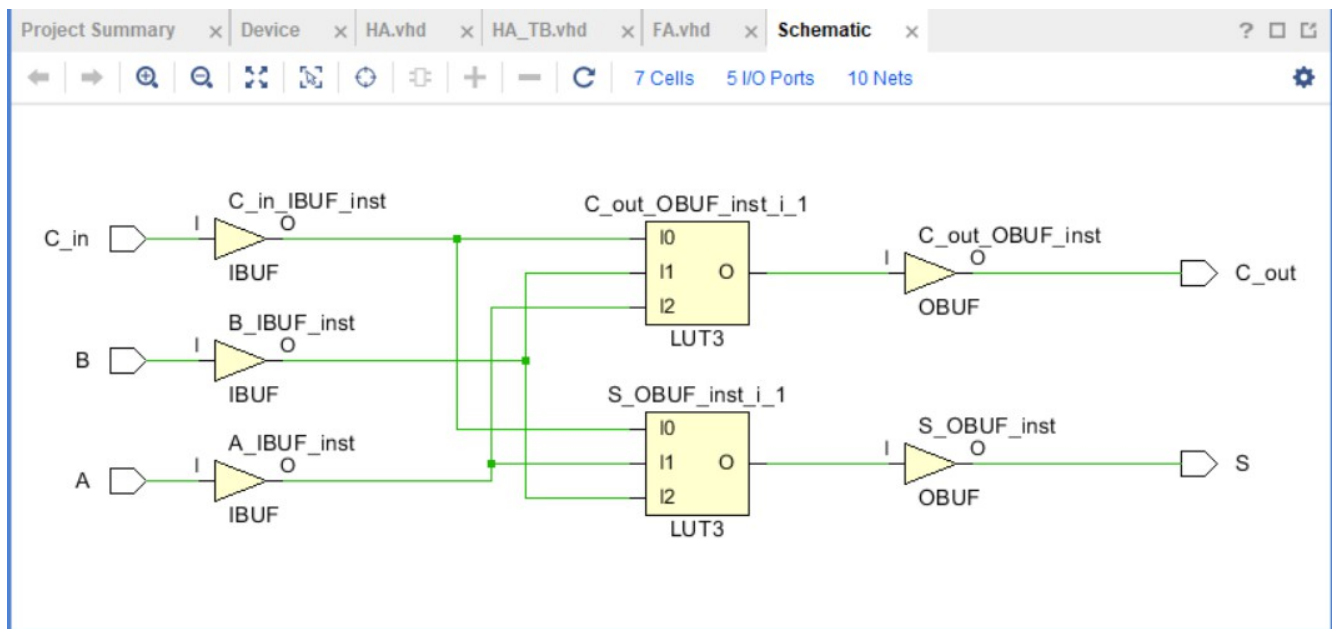

## 3-BIT\_ADDER

### Code

entity bit\_3\_adder is

Port ( A : in STD\_LOGIC\_VECTOR (2 downto 0);  
       S : out STD\_LOGIC\_VECTOR (2 downto 0)  
       );

end bit\_3\_adder;

architecture Behavioral of bit\_3\_adder is

component FA

port (  
     A: in std\_logic;  
     B: in std\_logic;  
     C\_in: in std\_logic;  
     S: out std\_logic;  
     C\_out: out std\_logic);

end component;

SIGNAL  
 FA0\_S, FA0\_C, FA1\_S, FA1\_C, FA2\_S, FA2\_C, FA3\_S, FA3\_C, C\_out1  
 : std\_logic;

begin

FA\_0 : FA

port map (  
     A => A(0),  
     B => '1',  
     C\_in => '0',  
     S => S(0),  
     C\_Out => FA0\_C);

FA\_1 : FA


```

port map (
  A => A(1),
  B => '0',
  C_in => FA0_C,
  S => S(1),
  C_Out => FA1_C);
FA_2 : FA
port map (
  A => A(2),
  B => '0',
  C_in => FA1_C,
  S => S(2),
  C_Out => C_out1);


```

end Behavioral;

## RTL

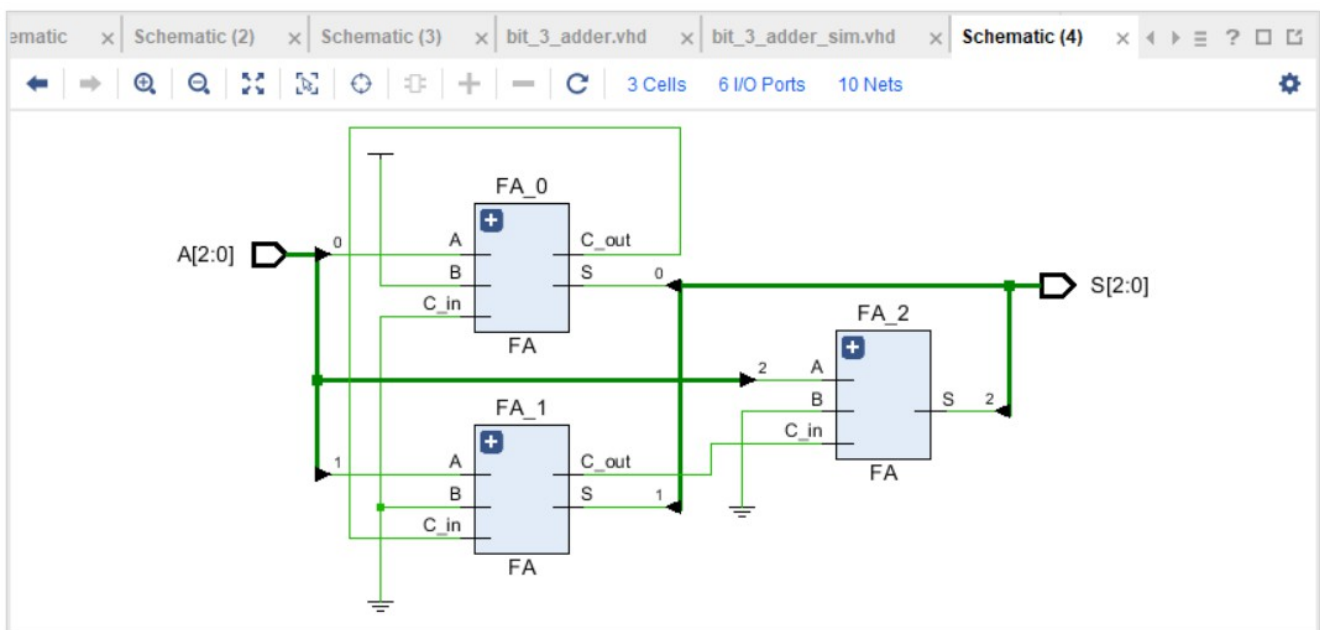

## Synthesized Design

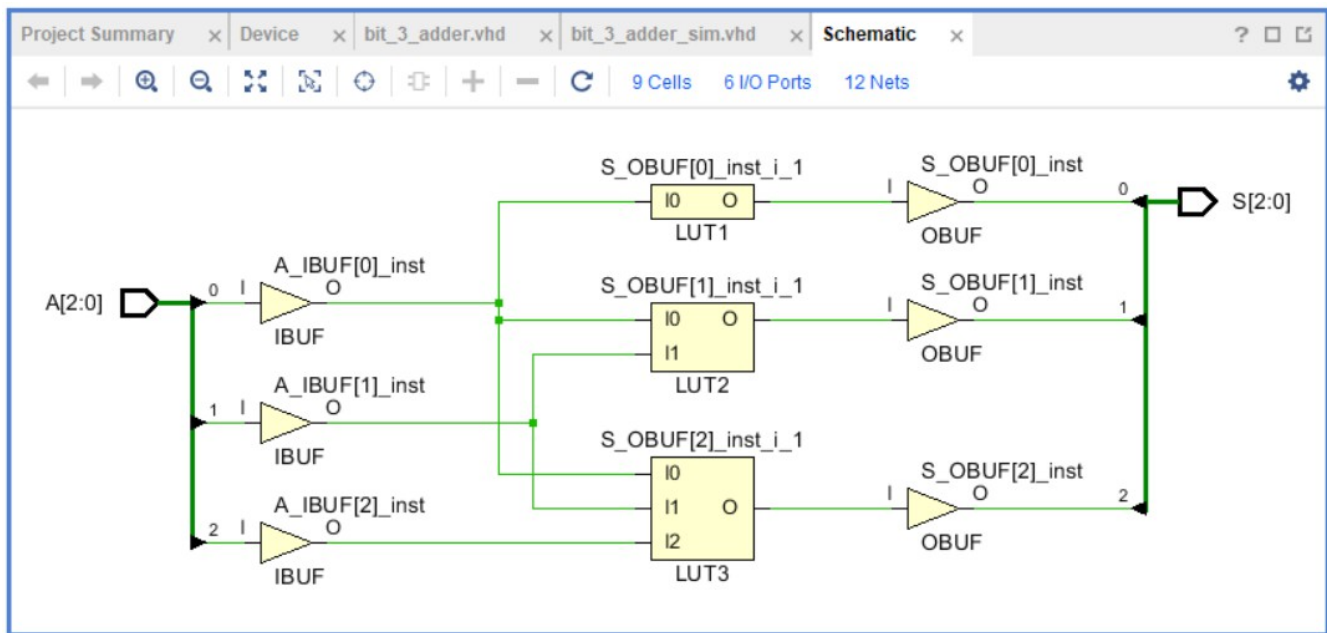

### Simulation Code

entity bit\_3\_adder\_sim is

end bit\_3\_adder\_sim;

architecture Behavioral of bit\_3\_adder\_sim is

component bit\_3\_adder

Port ( A : in STD\_LOGIC\_VECTOR (2 downto 0);

S : out STD\_LOGIC\_VECTOR (2 downto 0));

end component;

signal A : std\_logic\_vector (2 downto 0) := (others => '0');

signal S : std\_logic\_vector (2 downto 0 );

begin

uut : bit\_3\_adder port map

( A=> A,

S => S);

stiM\_PROC: PROCESS

BEGIN

A<= "000";

wait for 100 ns;

A<= "001";

wait for 100 ns;

A<= "010";



```

wait for 100 ns;
A<= "011";
wait for 100 ns;
A<= "100";
wait for 100 ns;
A<= "101";
wait for 100 ns;
A<= "110";
wait for 100 ns;
A<= "111";
wait;


```

```

end process;
end;

```

## Behavioral Simulation

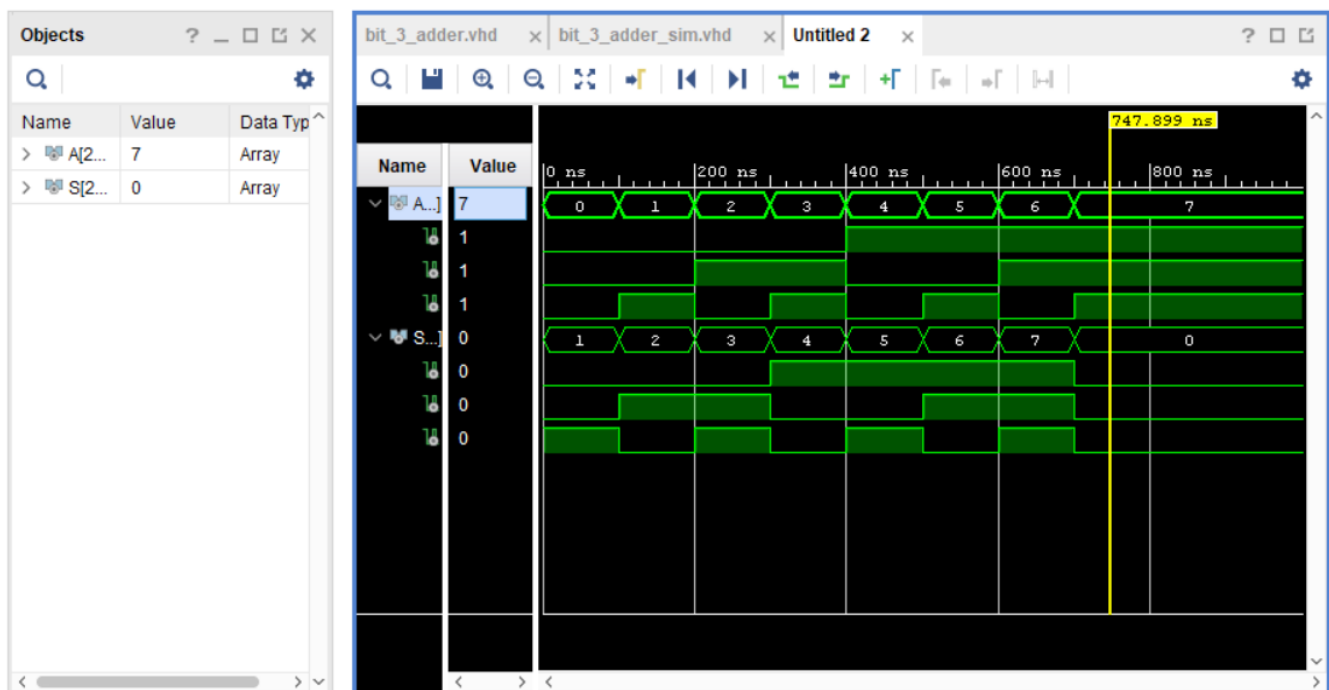

## Slow\_Clock

### Code

```

entity Slow_Clock is
  Port ( Clk_in : in STD_LOGIC;
         Clk_out : out STD_LOGIC);
end Slow_Clock;

architecture Behavioral of Slow_Clock is

```

```

signal count : integer := 1;
signal clk_status : std_logic := '0';

```

```

begin
  process (Clk_in) begin
    if (rising_edge(Clk_in)) then
      count <= count + 1;
      if (count = 50000000) then
        clk_status <= not clk_status;
        Clk_out <= clk_status;
        count <= 1;
      end if;
    end if;
  end process;


```

```


end Behavioral;

```

## RTL

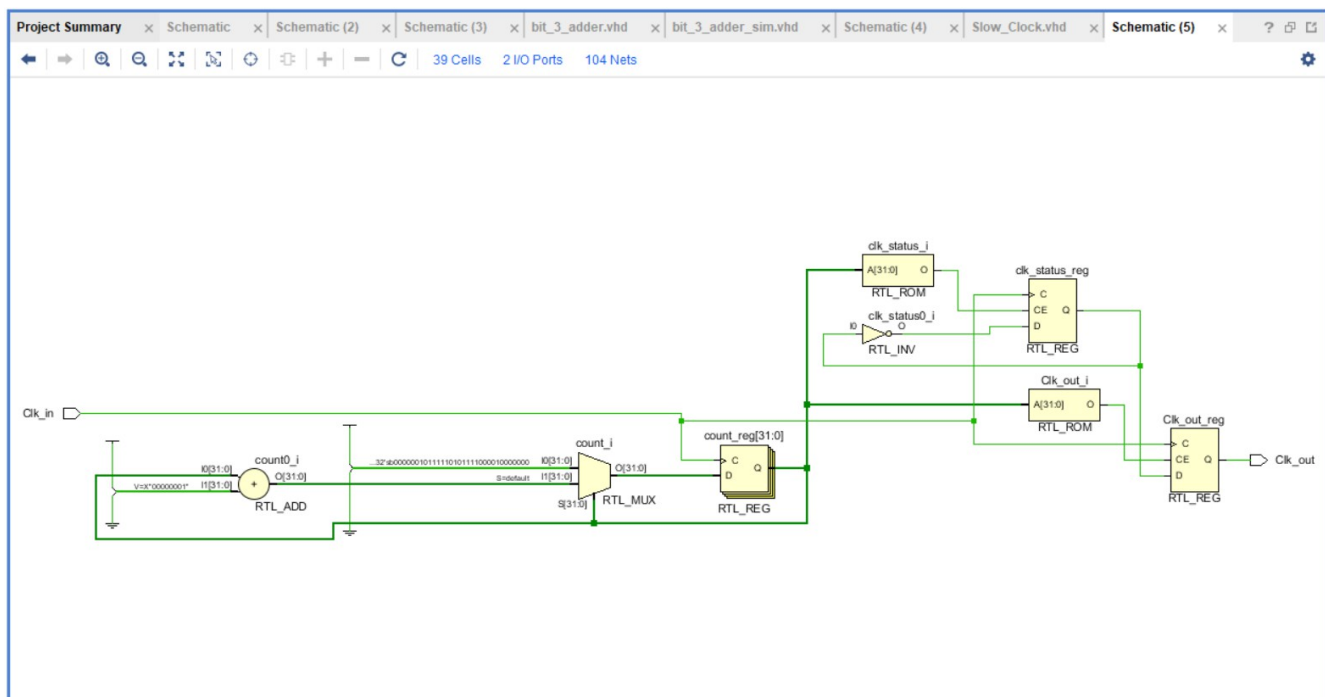

## Synthesized Design

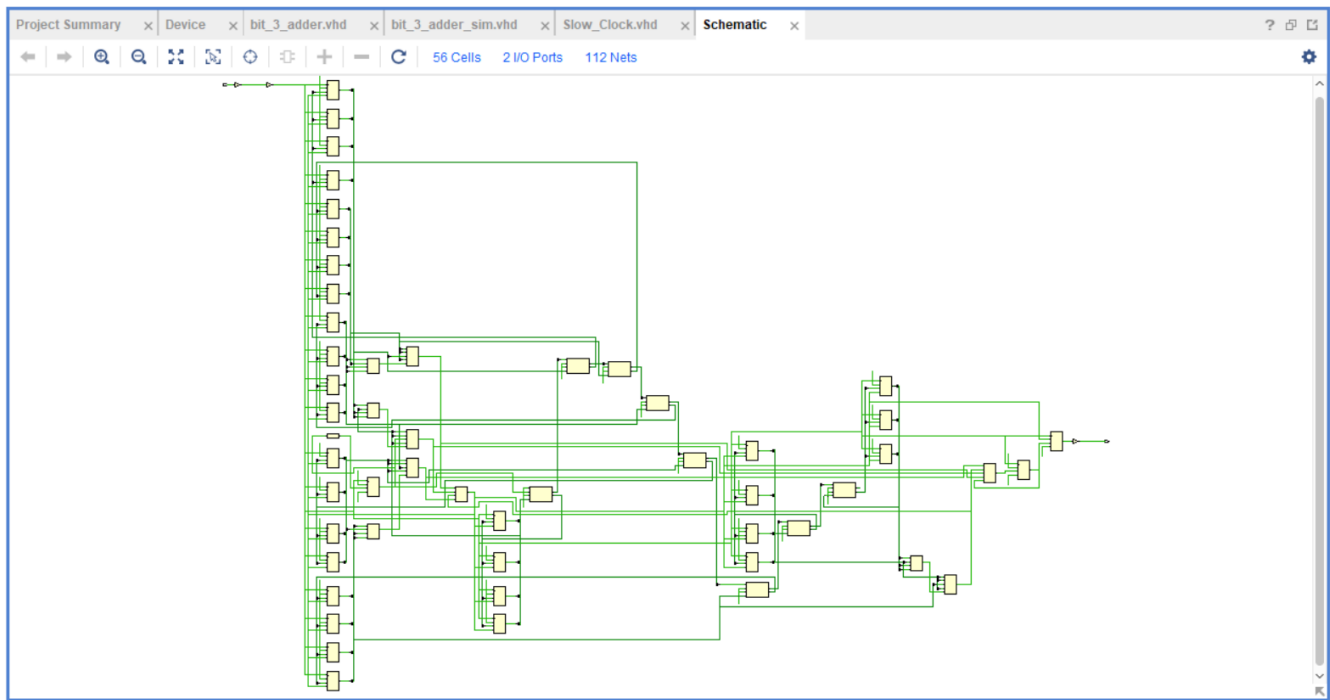

## 2 to 1 multiplexer

### Tables

S	D
0	D(0)
1	D(1)

### Code

entity mux2to1 is

```

    Port ( jumpsignal : in STD_LOGIC;
          bitt : in STD_LOGIC_VECTOR (1 downto 0);
          Outbit : out STD_LOGIC);
end mux2to1;
```


architecture Behavioral of mux2to1 is

begin


```
outbit <= (bitt(0)and (not jumpsignal)) or (bitt(1) and jumpsignal);
```

end Behavioral;

### RTL

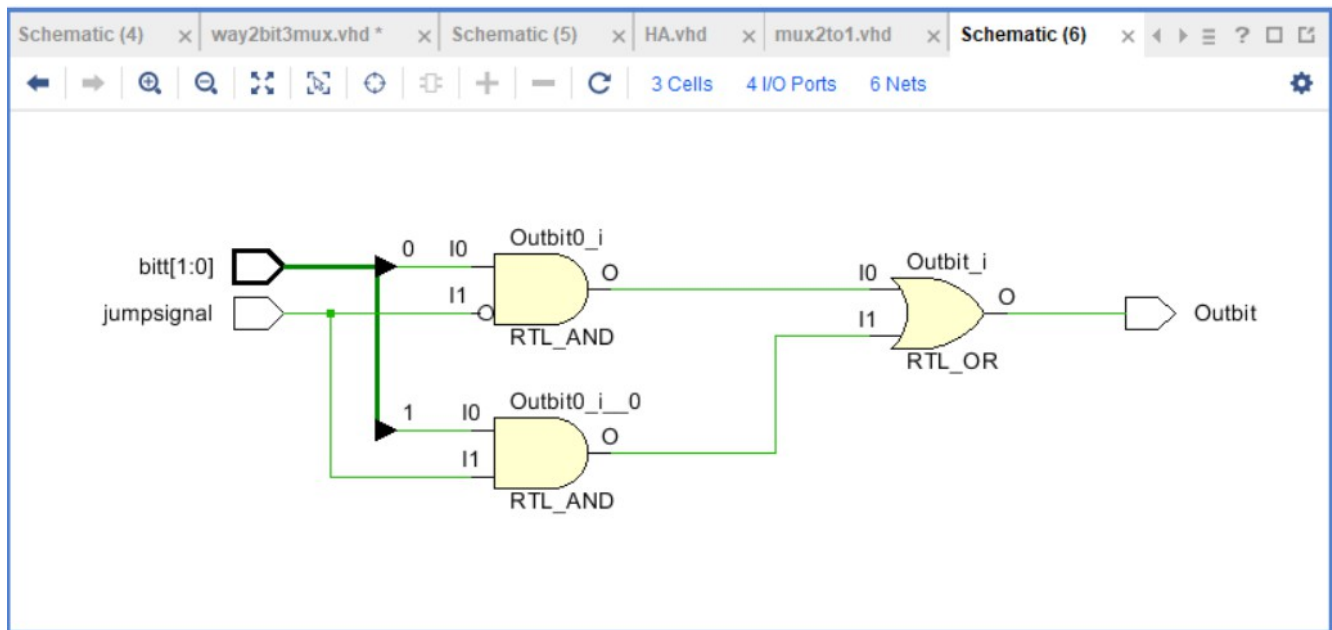

## Synthesized Design

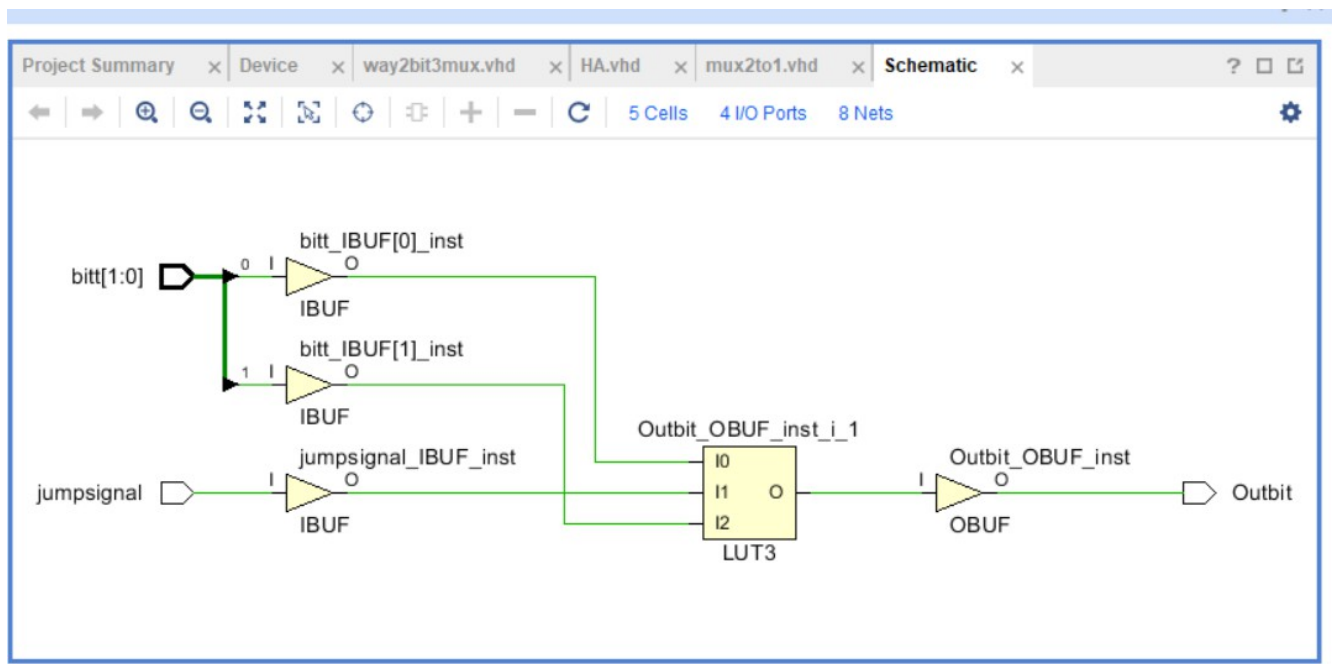

## 2 WAY 3 BIT MUX

### Code

entity way2bit3mux is

```
Port ( jumpflag : in STD_LOGIC;
      adresstojump : in STD_LOGIC_VECTOR (2 downto 0);
      default1 : in STD_LOGIC_VECTOR (2 downto 0);
```

```
        out1 : out STD_LOGIC_VECTOR (2 downto 0));  
end way2bit3mux;
```

architecture Behavioral of way2bit3mux is

component mux2to1

```
    Port ( jumpsignal : in STD_LOGIC;  
          bitt : in STD_LOGIC_VECTOR (1 downto 0);  
          Outbit : out STD_LOGIC);  
end component;
```

```
signal ha0_s, ha0_c, hal_c :std_logic;  
begin
```


```
MUX0 : mux2to1 PORT MAP (  
    jumpsignal => jumpflag,  
    bitt(0) => default1(0),  
    bitt(1) => adresstojump(0),  
    outbit => out1(0));
```

```
MUX1 : mux2to1 PORT MAP (  
    jumpsignal => jumpflag,  
    bitt(0) => default1(1),  
    bitt(1) => adresstojump(1),  
    outbit => out1(1));
```


```
MUX2 : mux2to1 PORT MAP (  
    jumpsignal => jumpflag,  
    bitt(0) => default1(2),  
    bitt(1) => adresstojump(2),  
    outbit => out1(2));
```

```
end Behavioral;
```

**RTL**

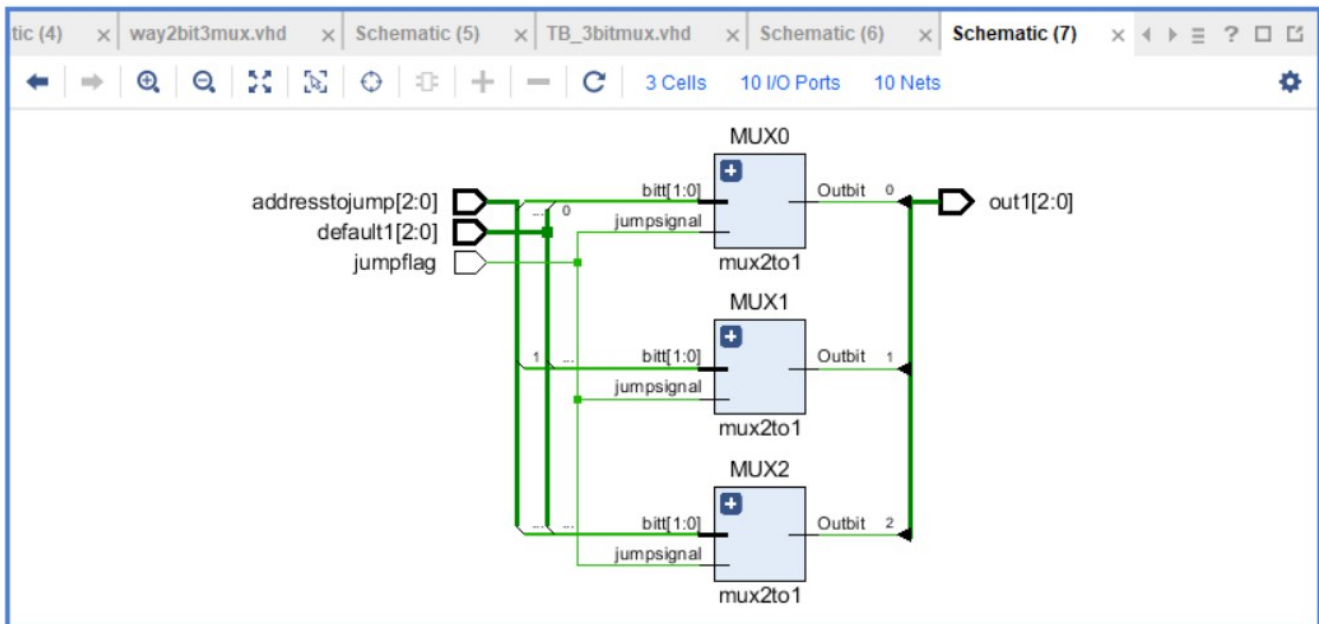

## Synthesized Design

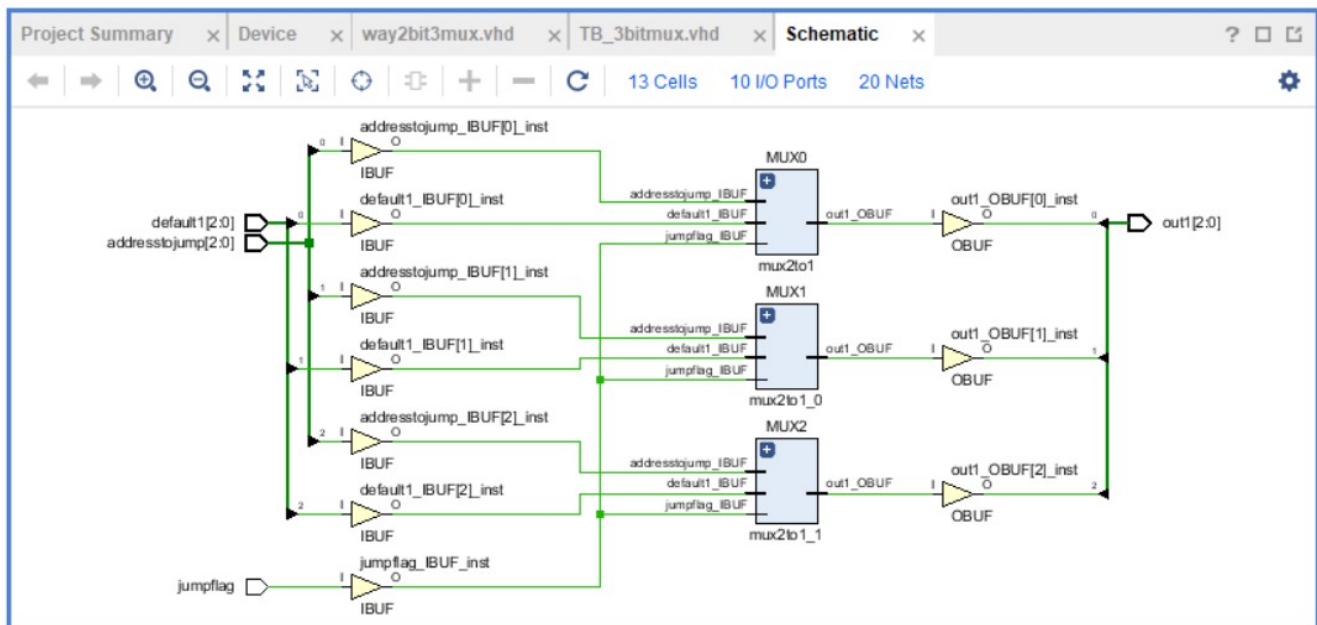

## Simulation\_Code

entity TB\_3bitmux is  
 -- Port ();  
end TB\_3bitmux;

architecture Behavioral of TB\_3bitmux is  
 component way2bit3mux

```

Port ( jumpflag : in STD_LOGIC;
      adresstojump : in STD_LOGIC_VECTOR (2 downto 0);
      default1 : in STD_LOGIC_VECTOR (2 downto 0);
      out1 : out STD_LOGIC_VECTOR (2 downto 0));
end component;

signal adresstojump : std_logic_vector (2 downto 0 ) := (others => '0');
signal default1 : std_logic_vector (2 downto 0 );
signal out1 : std_logic_vector (2 downto 0 );
signal jumpflag : std_logic;

begin
uut : way2bit3mux port map
( jumpflag => jumpflag,
  adresstojump => adresstojump,
  default1 => default1,
  out1 => out1);
stiM_PROC: PROCESS
BEGIN

jumpflag<='0';
adresstojump<="010";
default1<="101";
wait for 100 ns;

jumpflag<='1';
adresstojump<="010";
default1<="101";
wait for 100 ns;


jumpflag<='0';
adresstojump<="000";
default1<="111";
wait for 100 ns;

jumpflag<='1';
adresstojump<="000";
default1<="111";
wait;

end process;
end;

```

### **Behavioral Simulation**

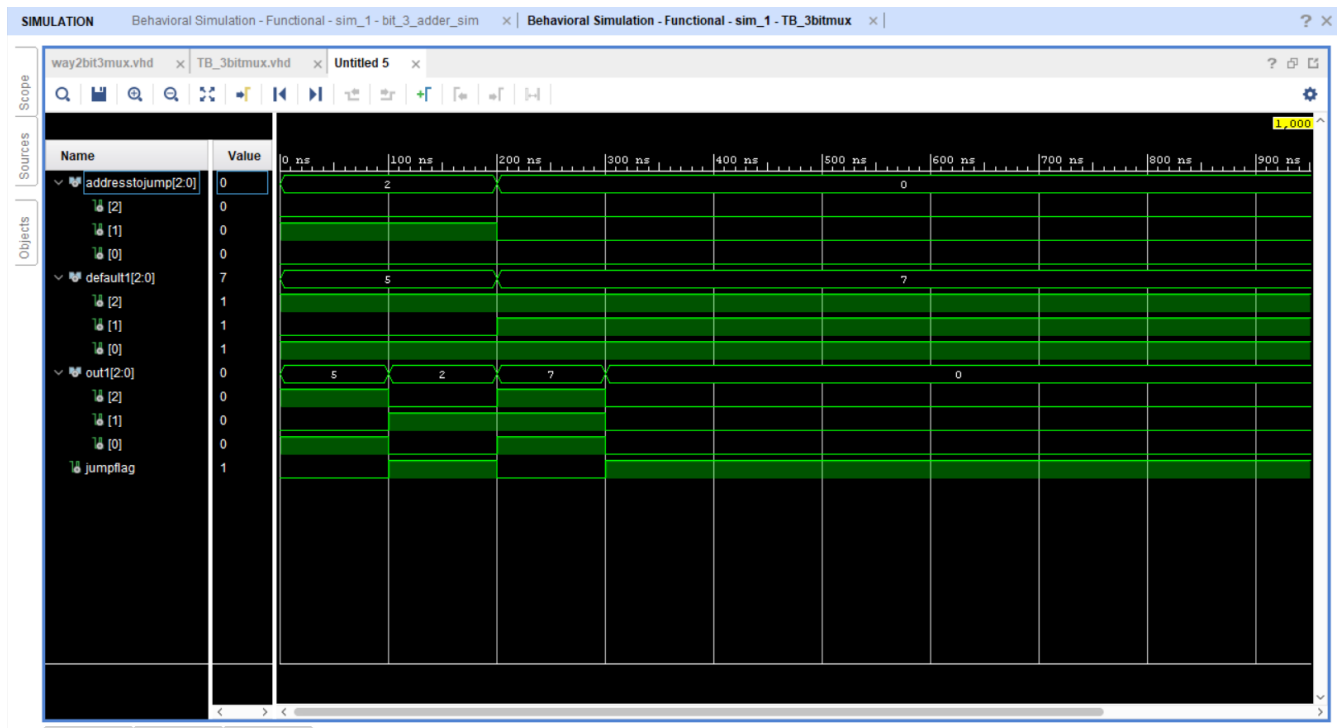

## D\_FF

### Code

entity D\_FF is

```
Port ( D : in STD_LOGIC;
      Res : in STD_LOGIC;
      Clk : in STD_LOGIC;
      Q : out STD_LOGIC;
      Qbar : out STD_LOGIC);
```

end D\_FF;

architecture Behavioral of D\_FF is

begin

process (Clk)

begin

if (rising\_edge (Clk)) then

if Res ='1' then

Q <= '0';

Qbar <= '1';

else

Q <=D;

Qbar <= not D;


end if;

end if;


end process;



end Behavioral;

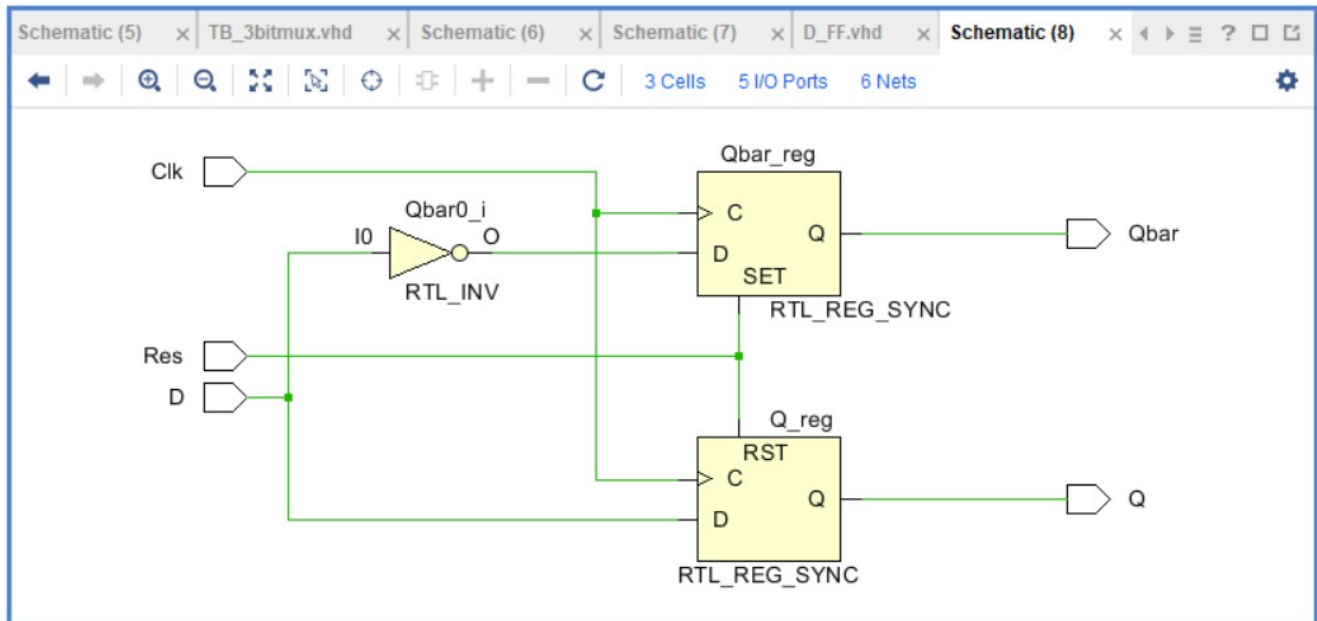RTL

### Synthesized Design

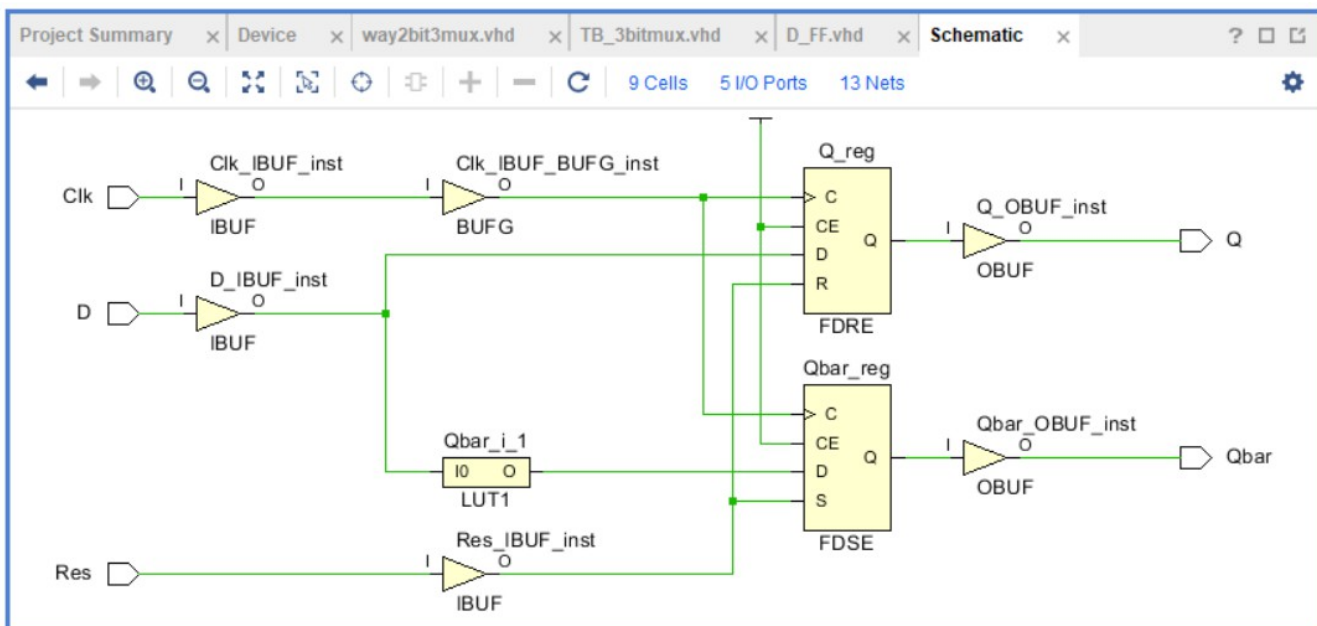

## Simulation Code

entity D\_FF\_Sim is

-- Port ();

end D\_FF\_Sim;

architecture Behavioral of D\_FF\_Sim is

component D\_FF

Port ( D : in STD\_LOGIC;

Res : in STD\_LOGIC;

Clk : in STD\_LOGIC;

Q : out STD\_LOGIC;

Qbar : out STD\_LOGIC);

end component;

signal D : std\_logic := '0';

signal Clk : std\_logic := '0';

signal Res : std\_logic := '1';

signal Q,Qbar : std\_logic;

constant clk\_period : time := 10 ns;

begin

uut: D\_FF port map(

D => D,

Res => Res,

Clk => Clk,

Q => Q,

Qbar => Qbar);

clk\_process :process

begin

Clk <='0';

wait for clk\_period/2;

Clk <='1';

wait for clk\_period/2;

end process;

stim\_proc : process

begin

Res <='1';

wait for 50 ns;

Res <='0';

D <='1';

wait for 50 ns;

Res <='0';

D <='0';

wait for 50 ns;

Res <='0';

D <='1';


```

wait for 50 ns;
Res <='1';
D <='1';
wait;
end process;

```

end Behavioral;

## Behavioral Simulation

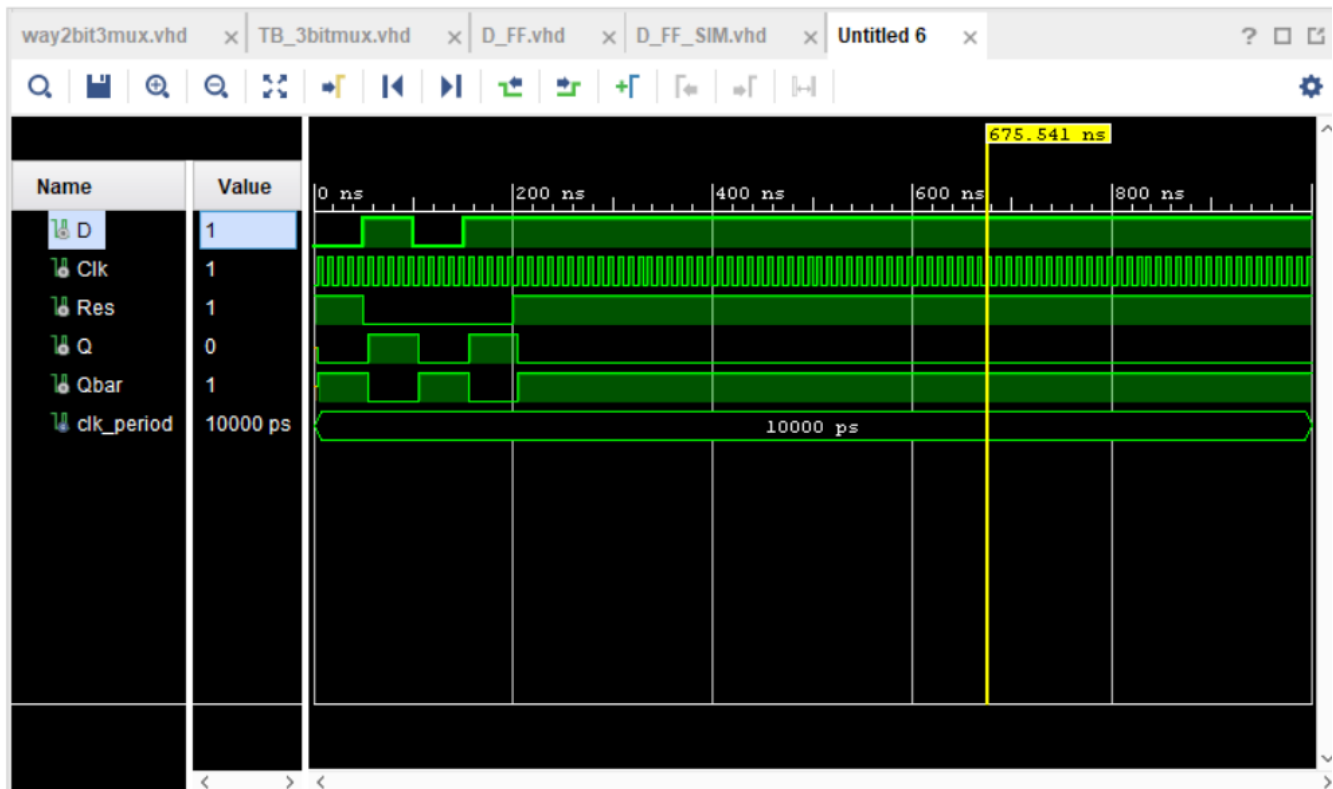

## Program Counter

### Code

```

entity PROGRAM_COUNTER is
  Port ( TOIN : in STD_LOGIC_VECTOR (2 downto 0);
        TOOOUT : out STD_LOGIC_VECTOR (2 downto 0);
        CLK : in STD_LOGIC;
        RES : in STD_LOGIC);
end PROGRAM_COUNTER;

```

architecture Behavioral of PROGRAM\_COUNTER is

```

component D_FF

```


```
Port ( D : in STD_LOGIC;  
      Res : in STD_LOGIC;  
      Clk : in STD_LOGIC;  
      Q : out STD_LOGIC;  
      Qbar : out STD_LOGIC);  
end component;
```

```
signal ha0_s :std_logic;  
begin
```


```
DFF0 : D_FF PORT MAP (  
    D => toin(0),  
    Res =>res,  
    Clk =>clk,  
    Q =>toout(0),  
    Qbar =>ha0_s);  
DFF1 : D_FF PORT MAP (  
    D => toin(1),  
    Res =>res,  
    Clk =>clk,  
    Q =>toout(1),  
    Qbar =>ha0_s);  
DFF2 : D_FF PORT MAP (  
    D => toin(2),  
    Res =>res,  
    Clk =>clk,  
    Q =>toout(2),  
    Qbar =>ha0_s);
```

```
end Behavioral;
```

**RTL**

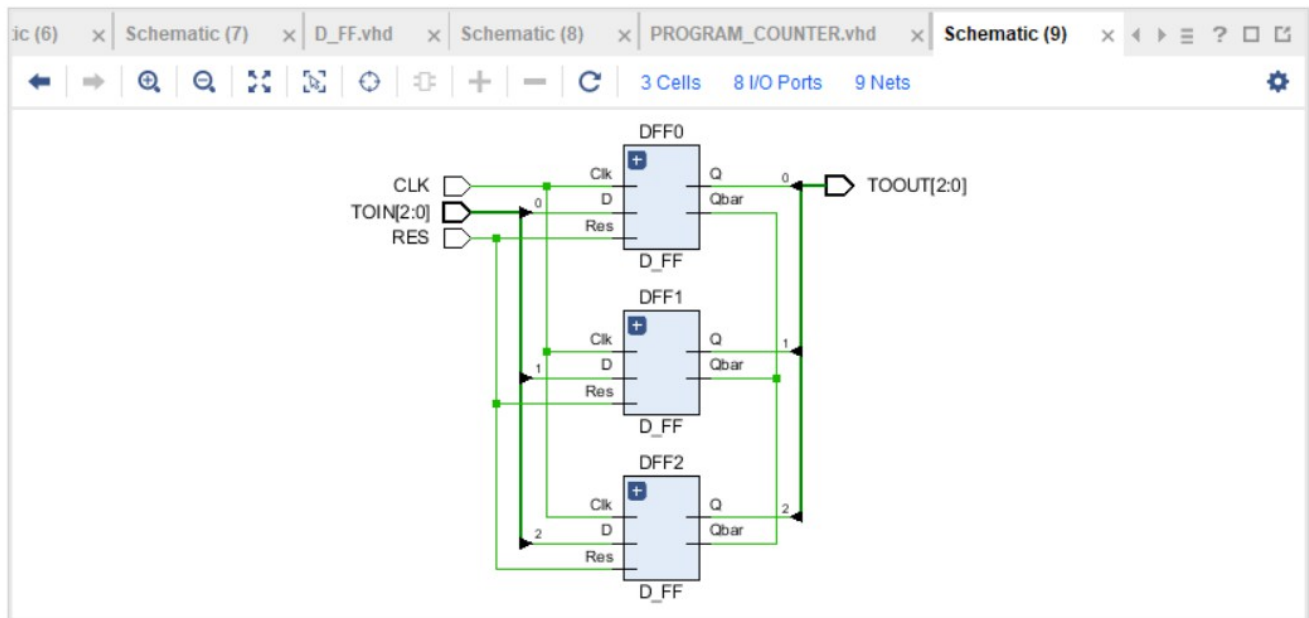

## Synthesized Design

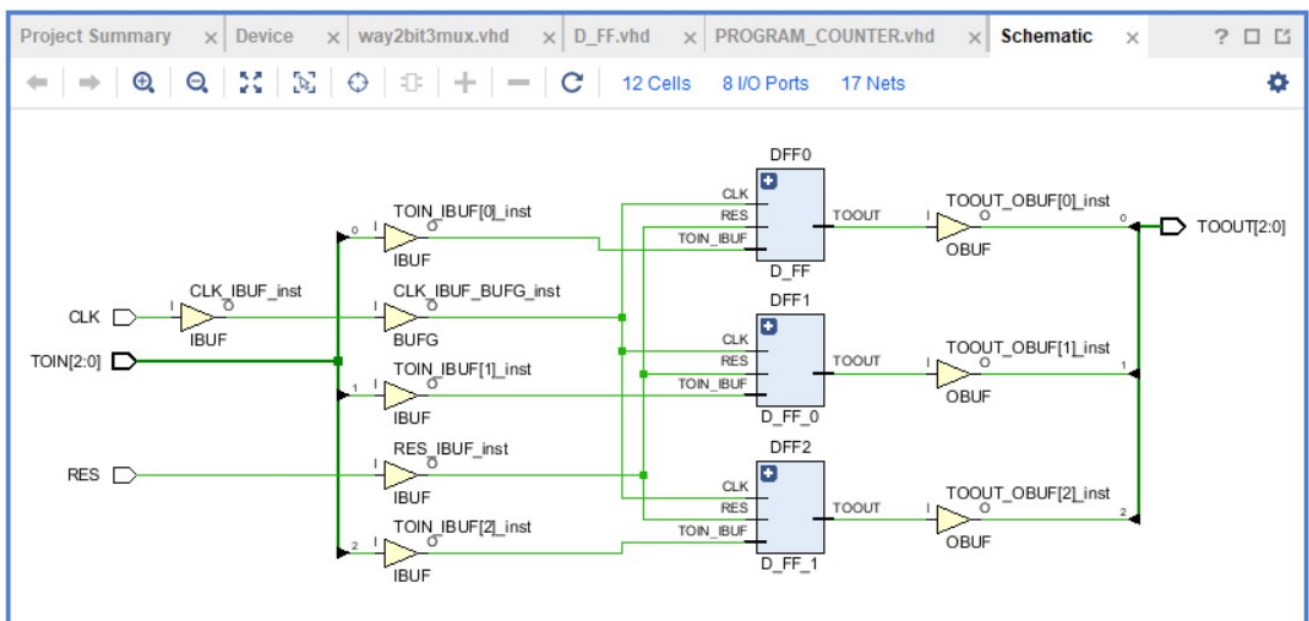

## Simulation Code

entity PC\_SIM is

-- Port ();

end PC\_SIM ;

architecture Behavioral of PC\_SIM is

```

component PROGRAM_COUNTER
Port ( TOIN : in STD_LOGIC_VECTOR (2 downto 0);
      TOOOUT : out STD_LOGIC_VECTOR (2 downto 0);
      CLK : in STD_LOGIC;
      RES : in STD_LOGIC);
end component;

```

```

signal TOIN : STD_LOGIC_VECTOR (2 downto 0);
signal TOOOUT : STD_LOGIC_VECTOR (2 downto 0);
signal CLK : STD_LOGIC;
signal RES : STD_LOGIC;

```

```

constant clk_period : time := 10 ns;

```


```

begin
uut: PROGRAM_COUNTER port map(
    TOOOUT => TOOOUT,
    TOIN => TOIN,
    CLK=>CLK,
    RES=>RES);
clk_process :process
begin
    Clk <='0';
    wait for clk_period/2;
    Clk <='1';
    wait for clk_period/2;
end process;
stim_proc : process
begin
    Res <='1';
    TOIN <="111";
    wait for 50 ns;
    Res <='1';
    TOIN <="000";
    wait for 50 ns;
    Res <='0';
    TOIN <="111";
    wait for 50 ns;
    Res <='0';
    TOIN <="000";
    wait;
end process;

end Behavioral;

```

### **Behavioral Simulation**

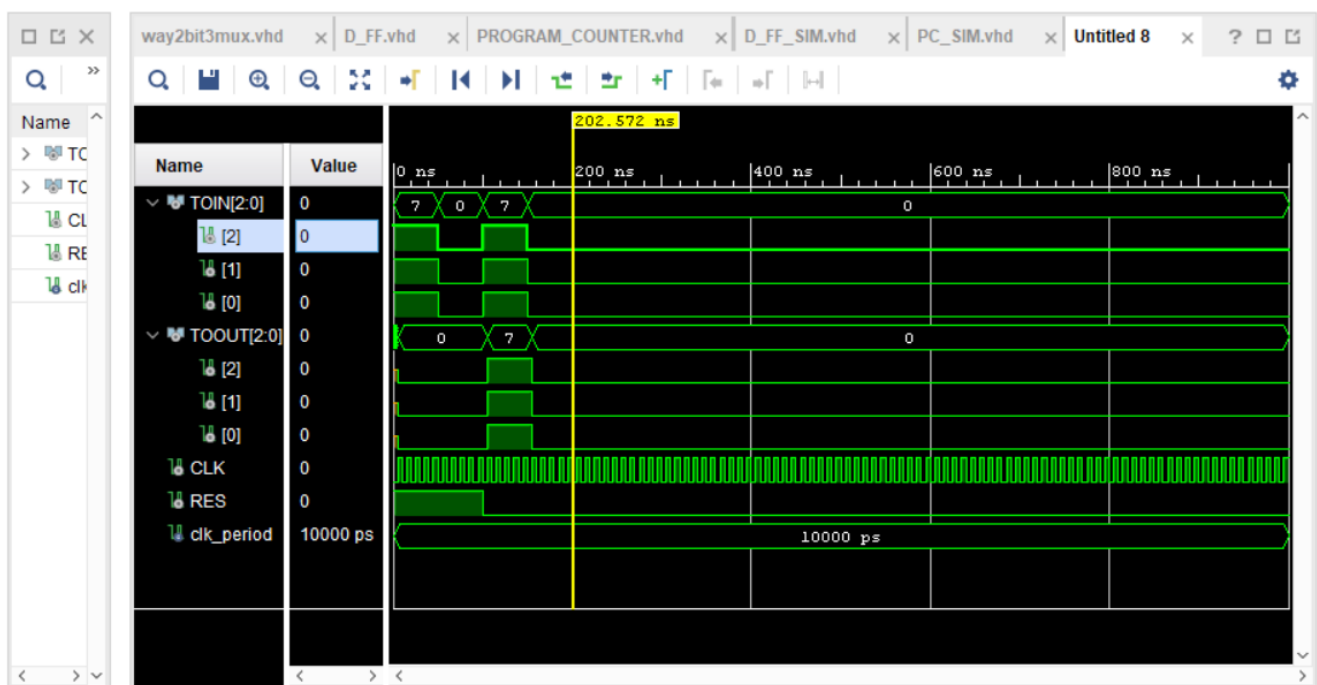

## 8 to 1 MUX

### Code

entity MUX8TO1 is

Port ( INTO : in STD\_LOGIC\_VECTOR (7 downto 0);

SEL : in STD\_LOGIC\_VECTOR (2 downto 0);

OUTTO : out STD\_LOGIC);

end MUX8TO1;

architecture Behavioral of MUX8TO1 is

signal ou,sel0,sel0b ,sel1,sel1b,sel2,sel2b,inter0,inter1,inter2,inter3,inter4,inter5,inter6,inter7  
:std\_logic;

begin

SEL0<=sel(0);

sel0b<=not sel(0);

sel1<=sel(1);

sel1b<=not sel(1);

sel2 <= sel(2);

sel2b<=not sel(2);

inter0<=into(0) and sel1b and sel2b and sel0b;

inter1<=into(1) and sel0 and sel1b and sel2b;

inter2<=into(2) and sel2b and sel1 and sel0b;

inter3<=into(3) and sel2b and sel1 and sel0;

```

inter4<=into(4) and sel2 and sel1b and sel0b;
inter5<=into(5) and sel2 and sel1b and sel0;
inter6<=into(6) and sel2 and sel1 and sel0b;
inter7<=into(7) and sel2 and sel1 and sel0;


```

```

ou<=inter0 or inter1 or inter2 or inter3 or inter4 or inter5 or inter6 or inter7;
outto<=ou;
end Behavioral;


```

## RTL

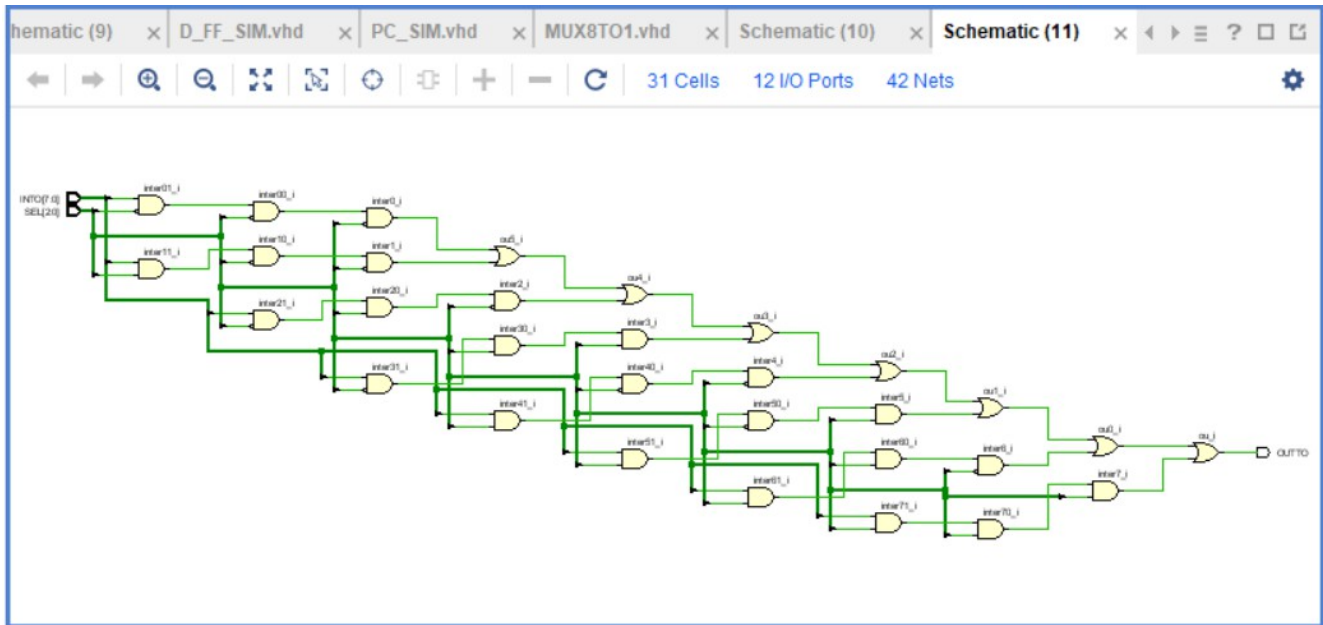

## Synthesized Design



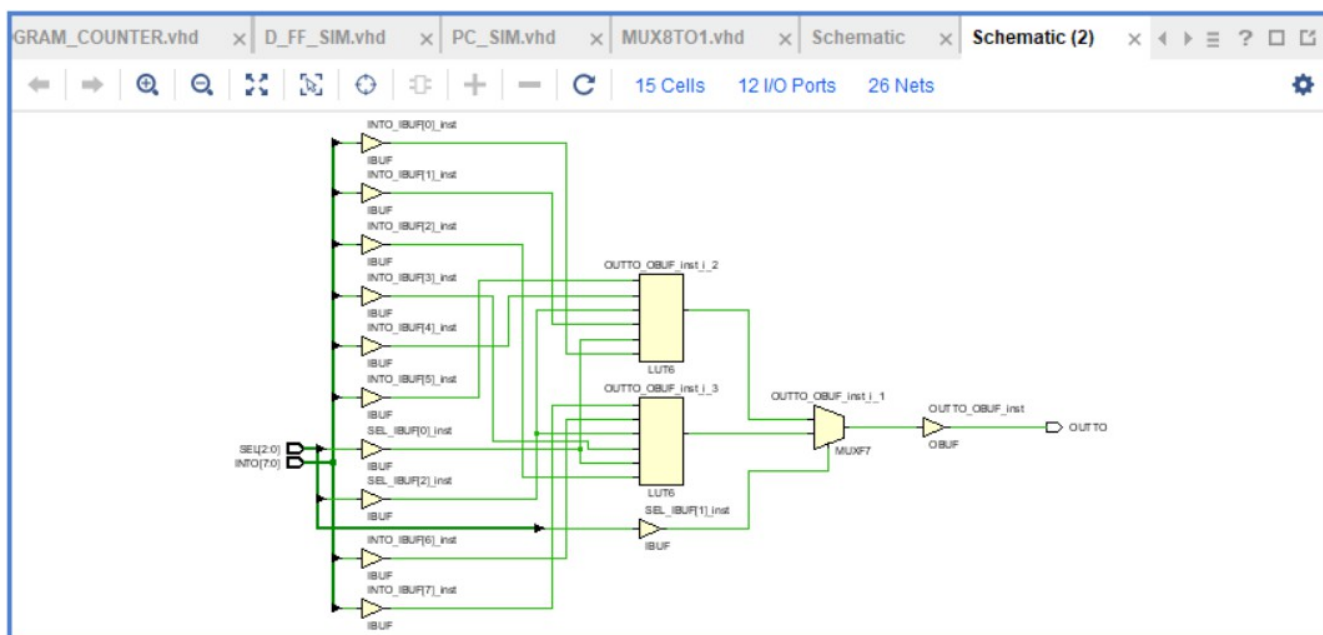

## 8 WAY 4 BIT MUX

### Code

entity way8bit4mux is

```
Port ( regsel : in STD_LOGIC_VECTOR (2 downto 0);
      reg0 : in STD_LOGIC_VECTOR (3 downto 0);
      reg1 : in STD_LOGIC_VECTOR (3 downto 0);
      reg2 : in STD_LOGIC_VECTOR (3 downto 0);
      reg3 : in STD_LOGIC_VECTOR (3 downto 0);
      reg4 : in STD_LOGIC_VECTOR (3 downto 0);
      reg5 : in STD_LOGIC_VECTOR (3 downto 0);
      reg6 : in STD_LOGIC_VECTOR (3 downto 0);
      reg7 : in STD_LOGIC_VECTOR (3 downto 0);
      out1 : out STD_LOGIC_VECTOR (3 downto 0));
```

end way8bit4mux;

architecture Behavioral of way8bit4mux is

component mux8to1

```
Port ( INTO : in STD_LOGIC_VECTOR (7 downto 0);
      SEL : in STD_LOGIC_VECTOR (2 downto 0);
      OUTTO : out STD_LOGIC);
```

end component;

```
signal ha0_s, ha0_c, hal_c :std_logic;
begin
```

```
MUX0 : mux8to1 PORT MAP (
  sel => regsel,
```


```
into(0)=> reg0(0),
into(1)=> reg1(0),
into(2)=> reg2(0),
into(3)=> reg3(0),
into(4)=> reg4(0),
into(5)=> reg5(0),
into(6)=> reg6(0),
into(7)=> reg7(0),
outto=>out1(0));
```

```
MUX1 : mux8to1 PORT MAP (
    sel => regsel,
    into(0)=> reg0(1),
    into(1)=> reg1(1),
    into(2)=> reg2(1),
    into(3)=> reg3(1),
    into(4)=> reg4(1),
    into(5)=> reg5(1),
    into(6)=> reg6(1),
    into(7)=> reg7(1),
    outto=>out1(1));
```


```
MUX2 : mux8to1 PORT MAP (
    sel => regsel,
    into(0)=> reg0(2),
    into(1)=> reg1(2),
    into(2)=> reg2(2),
    into(3)=> reg3(2),
    into(4)=> reg4(2),
    into(5)=> reg5(2),
    into(6)=> reg6(2),
    into(7)=> reg7(2),
    outto=>out1(2));
```

```
MUX3 : mux8to1 PORT MAP (
    sel => regsel,
    into(0)=> reg0(3),
    into(1)=> reg1(3),
    into(2)=> reg2(3),
    into(3)=> reg3(3),
    into(4)=> reg4(3),
    into(5)=> reg5(3),
    into(6)=> reg6(3),
    into(7)=> reg7(3),
    outto=>out1(3));
end Behavioral;
```

**RTL**

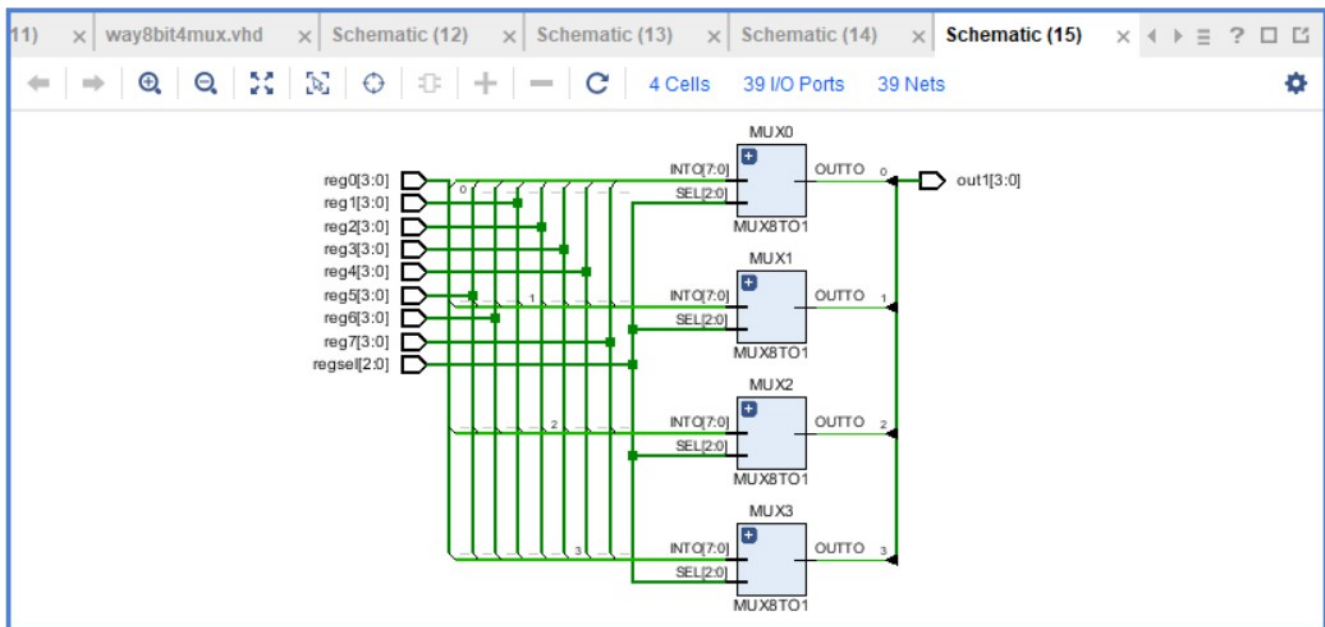

## Synthesized Design

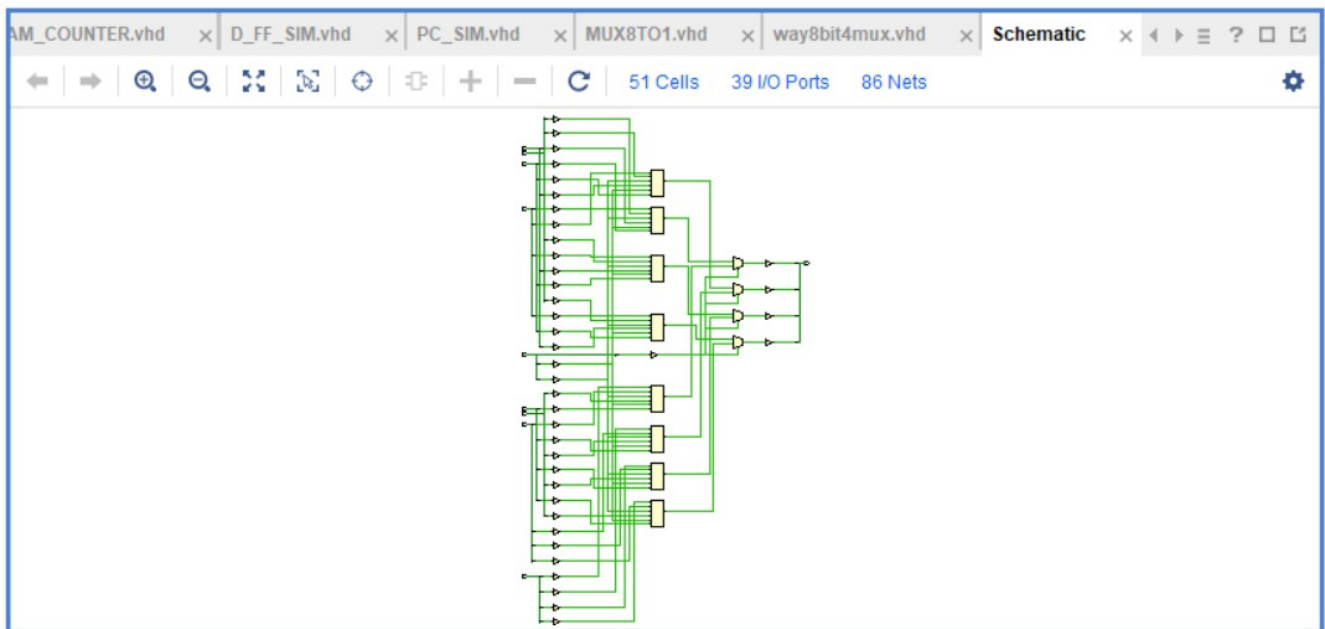

## Simulation\_Code

```
entity sim_4_bit_mux is
-- Port ();
end sim_4_bit_mux;
```

```
architecture Behavioral of sim_4_bit_mux is
```

component way8bit4mux

```
Port (  regsel : in STD_LOGIC_VECTOR (2 downto 0);
      reg0 : in STD_LOGIC_VECTOR (3 downto 0);
      reg1 : in STD_LOGIC_VECTOR (3 downto 0);
      reg2 : in STD_LOGIC_VECTOR (3 downto 0);
      reg3 : in STD_LOGIC_VECTOR (3 downto 0);
      reg4 : in STD_LOGIC_VECTOR (3 downto 0);
      reg5 : in STD_LOGIC_VECTOR (3 downto 0);
      reg6 : in STD_LOGIC_VECTOR (3 downto 0);
      reg7 : in STD_LOGIC_VECTOR (3 downto 0);
      out1 : out STD_LOGIC_VECTOR (3 downto 0));
```

end component;

```
signal regsel : STD_LOGIC_VECTOR (2 downto 0);
signal reg0 : STD_LOGIC_VECTOR (3 downto 0);
signal reg1 : STD_LOGIC_VECTOR (3 downto 0);
signal reg2 : STD_LOGIC_VECTOR (3 downto 0);
signal reg3 : STD_LOGIC_VECTOR (3 downto 0);
signal reg4 : STD_LOGIC_VECTOR (3 downto 0);
signal reg5 : STD_LOGIC_VECTOR (3 downto 0);
signal reg6 : STD_LOGIC_VECTOR (3 downto 0);
signal reg7 : STD_LOGIC_VECTOR (3 downto 0);
signal out1 : STD_LOGIC_VECTOR (3 downto 0);
```

begin

```
uut : way8bit4mux port map(
    regsel =>regsel,
    reg0 =>reg0,
    reg1 =>reg1,
    reg2 =>reg2,
    reg3 =>reg3,
    reg4 =>reg4,
    reg5 =>reg5,
    reg6 =>reg6,
    reg7 =>reg7,
    out1 =>out1);
```

```
stim_PROC: PROCESS
BEGIN
```

```
reg0 <= "0000";
reg1 <= "0000";
reg2 <= "0000";
reg3 <= "0000";
reg4 <= "0000";
reg5 <= "0000";
```

```
reg6 <= "0000";  
reg7 <= "0000";
```

```
regsel <= "000";  
reg0 <= "0111";  
wait for 100 ns;
```

```
regsel <= "001";  
reg1 <= "0100";  
wait for 100 ns;
```

```
regsel <= "010";  
reg2 <= "0111";  
wait for 100 ns;
```

```
regsel <= "011";  
reg3 <= "0100";  
wait for 100 ns;
```

```
regsel <= "100";  
reg4 <= "1010";  
wait for 100 ns;
```


```
regsel <= "101";  
reg5 <= "1111";  
wait for 100 ns;
```

```
regsel <= "110";  
reg6 <= "0100";  
wait for 100 ns;
```

```
regsel <= "111";  
reg7 <= "1110";  
wait;
```

```
end process;  
end;
```

### **Behavioral Simulation**

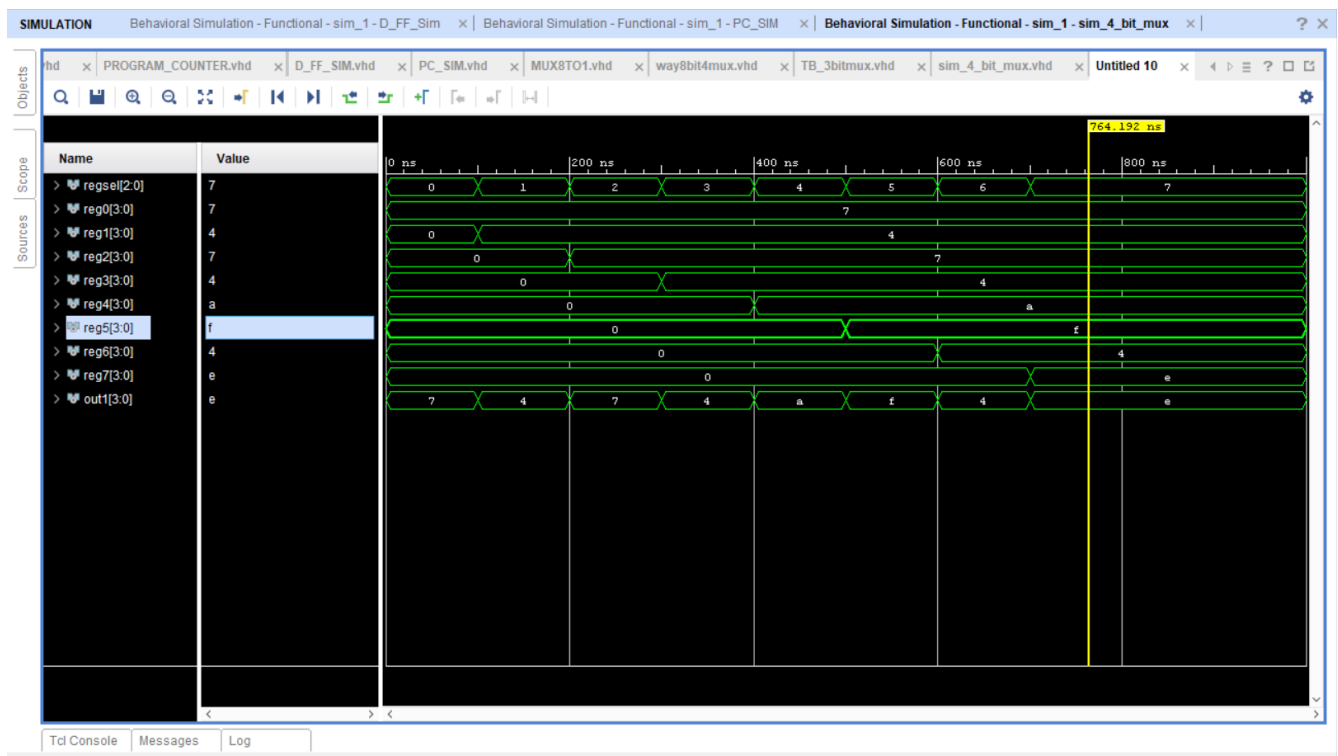

## Program ROM

### Code

```
entity program_rom is
    Port ( regsel : in STD_LOGIC_VECTOR (2 downto 0);
          out1 : out STD_LOGIC_VECTOR (11 downto 0));
end program_rom;
```

architecture Behavioral of program\_rom is

```
component mux8to1
    Port ( INTO : in STD_LOGIC_VECTOR (7 downto 0);
          SEL : in STD_LOGIC_VECTOR (2 downto 0);
          OUTTO : out STD_LOGIC);
end component;
```

```
type rom_type is array (0 to 7) of std_logic_vector (11 downto 0);
signal ROM : rom_type :=(
    "111111111111",----gfedcba---0
    "111111111111",---1
    "111111111111",---2
    "111111111111",---3
    "111111111111",--4
    "111111111111",---5
    "111111111111",---6
    "111111111111",---7
```

);

begin

```
MUX0 : mux8to1 PORT MAP (  
    sel => regsel,  
    into(0)=> rom(0)(0),  
    into(1)=> rom(1)(0),  
    into(2)=> rom(2)(0),  
    into(3)=> rom(3)(0),  
    into(4)=> rom(4)(0),  
    into(5)=> rom(5)(0),  
    into(6)=> rom(6)(0),  
    into(7)=> rom(7)(0),  
    outto=>out1(0));
```

```
MUX1 : mux8to1 PORT MAP (  
    sel => regsel,  
    into(0)=> rom(0)(1),  
    into(1)=> rom(1)(1),  
    into(2)=> rom(2)(1),  
    into(3)=> rom(3)(1),  
    into(4)=> rom(4)(1),  
    into(5)=> rom(5)(1),  
    into(6)=> rom(6)(1),  
    into(7)=> rom(7)(1),  
    outto=>out1(1));
```

```
MUX2 : mux8to1 PORT MAP (  
    sel => regsel,  
    into(0)=> rom(0)(2),  
    into(1)=> rom(1)(2),  
    into(2)=> rom(2)(2),  
    into(3)=> rom(3)(2),  
    into(4)=> rom(4)(2),  
    into(5)=> rom(5)(2),  
    into(6)=> rom(6)(2),  
    into(7)=> rom(7)(2),  
    outto=>out1(2));
```

```
MUX3 : mux8to1 PORT MAP (  
    sel => regsel,  
    into(0)=> rom(0)(3),  
    into(1)=> rom(1)(3),  
    into(2)=> rom(2)(3),  
    into(3)=> rom(3)(3),  
    into(4)=> rom(4)(3),  
    into(5)=> rom(5)(3),  
    into(6)=> rom(6)(3),  
    into(7)=> rom(7)(3),  
    outto=>out1(3));
```

```

MUX4 : mux8to1 PORT MAP (
    sel => regsel,
    into(0)=> rom(0)(4),
    into(1)=> rom(1)(4),
    into(2)=> rom(2)(4),
    into(3)=> rom(3)(4),
    into(4)=> rom(4)(4),
    into(5)=> rom(5)(4),
    into(6)=> rom(6)(4),
    into(7)=> rom(7)(4),
    outto=>out1(4));
MUX5 : mux8to1 PORT MAP (
    sel => regsel,
    into(0)=> rom(0)(5),
    into(1)=> rom(1)(5),
    into(2)=> rom(2)(5),
    into(3)=> rom(3)(5),
    into(4)=> rom(4)(5),
    into(5)=> rom(5)(5),
    into(6)=> rom(6)(5),
    into(7)=> rom(7)(5),
    outto=>out1(5));
MUX6 : mux8to1 PORT MAP (
    sel => regsel,
    into(0)=> rom(0)(6),
    into(1)=> rom(1)(6),
    into(2)=> rom(2)(6),
    into(3)=> rom(3)(6),
    into(4)=> rom(4)(6),
    into(5)=> rom(5)(6),
    into(6)=> rom(6)(6),
    into(7)=> rom(7)(6),
    outto=>out1(6));
MUX7 : mux8to1 PORT MAP (
    sel => regsel,
    into(0)=> rom(0)(7),
    into(1)=> rom(1)(7),
    into(2)=> rom(2)(7),
    into(3)=> rom(3)(7),
    into(4)=> rom(4)(7),
    into(5)=> rom(5)(7),
    into(6)=> rom(6)(7),
    into(7)=> rom(7)(7),
    outto=>out1(7));
MUX8 : mux8to1 PORT MAP (
    sel => regsel,
    into(0)=> rom(0)(8),
    into(1)=> rom(1)(8),
    into(2)=> rom(2)(8),

```




```


        into(3)=> rom(3)(8),
        into(4)=> rom(4)(8),
        into(5)=> rom(5)(8),
        into(6)=> rom(6)(8),
        into(7)=> rom(7)(8),
        outto=>out1(8));
MUX9 : mux8to1 PORT MAP (
    sel => regsel,
    into(0)=> rom(0)(9),
    into(1)=> rom(1)(9),
    into(2)=> rom(2)(9),
    into(3)=> rom(3)(9),
    into(4)=> rom(4)(9),
    into(5)=> rom(5)(9),
    into(6)=> rom(6)(9),
    into(7)=> rom(7)(9),
    outto=>out1(9));
MUX10 : mux8to1 PORT MAP (
    sel => regsel,
    into(0)=> rom(0)(10),
    into(1)=> rom(1)(10),
    into(2)=> rom(2)(10),
    into(3)=> rom(3)(10),
    into(4)=> rom(4)(10),
    into(5)=> rom(5)(10),
    into(6)=> rom(6)(10),
    into(7)=> rom(7)(10),
    outto=>out1(10));
MUX11 : mux8to1 PORT MAP (
    sel => regsel,
    into(0)=> rom(0)(11),
    into(1)=> rom(1)(11),
    into(2)=> rom(2)(11),
    into(3)=> rom(3)(11),
    into(4)=> rom(4)(11),
    into(5)=> rom(5)(11),
    into(6)=> rom(6)(11),
    into(7)=> rom(7)(11),
    outto=>out1(11));
end Behavioral;

```

**RTL**

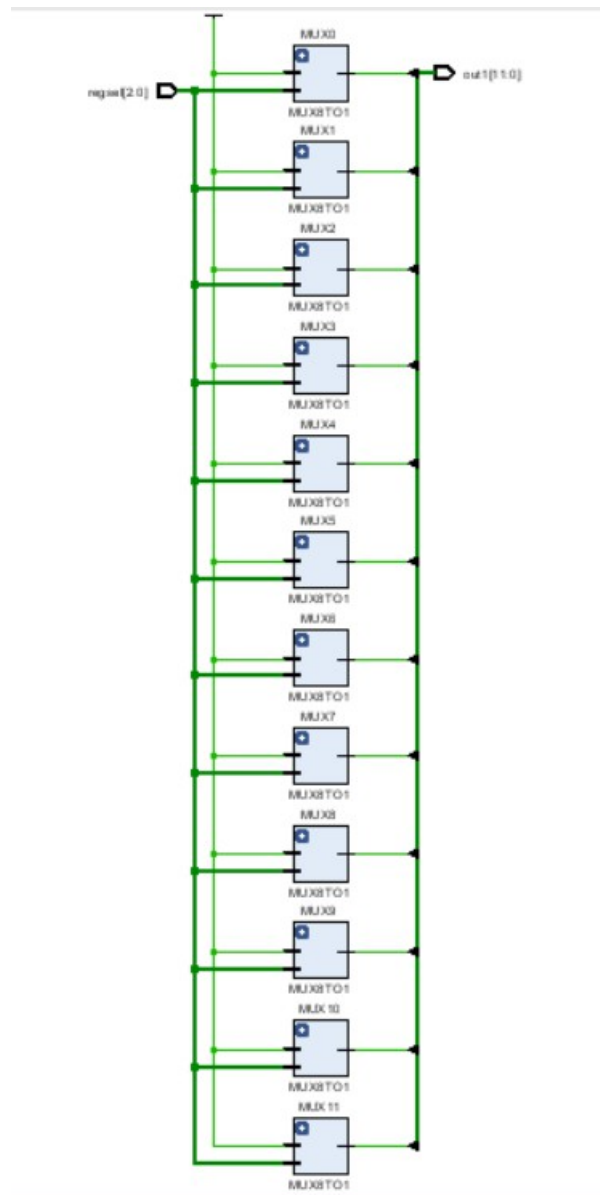

## Synthesized Design

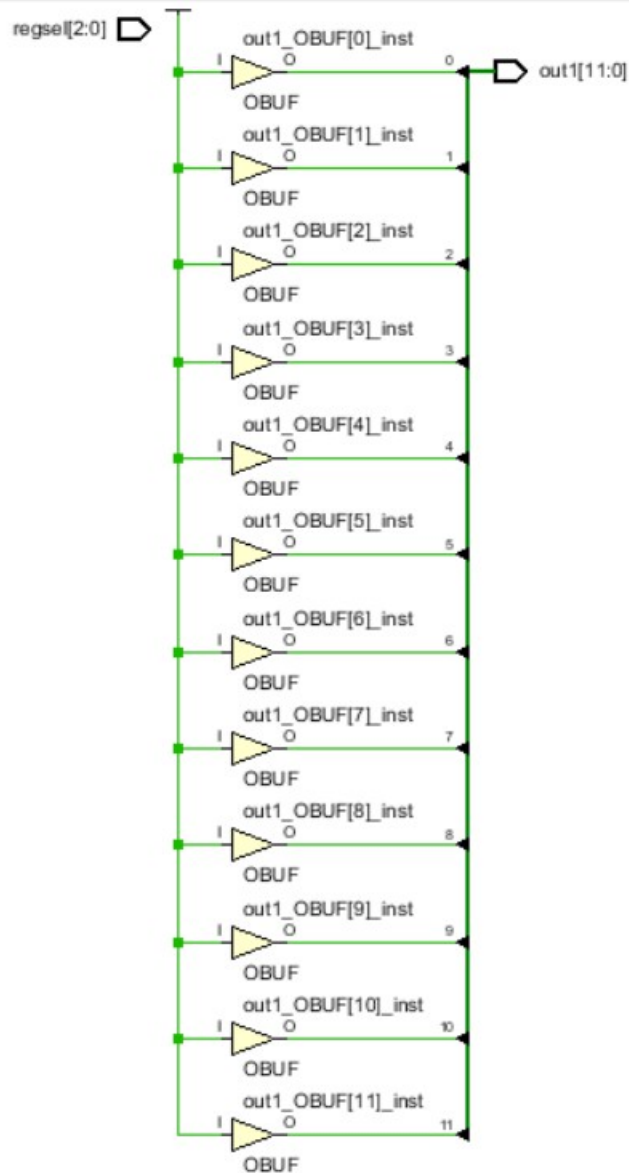

### Simulation\_Code

```
entity TB_Programrom is
-- Port ();
end TB_Programrom;
```

```
architecture Behavioral of TB_Programrom is
component program_rom
```

```
Port ( regsel : in STD_LOGIC_VECTOR (2 downto 0);
      out1 : out STD_LOGIC_VECTOR (11 downto 0));
```

```
end component;
```

```
signal regsel : STD_LOGIC_VECTOR (2 downto 0);
signal out1 : STD_LOGIC_VECTOR (11 downto 0);
```

```
begin

uut : program_rom port map(
    regsel =>regsel,
    out1 =>out1);


stiM_PROC: PROCESS
BEGIN

    regsel <= "110";
    wait for 100 ns;

    regsel <= "111";
    wait;

end process;
end;
```

### **Behavioral Simulation**

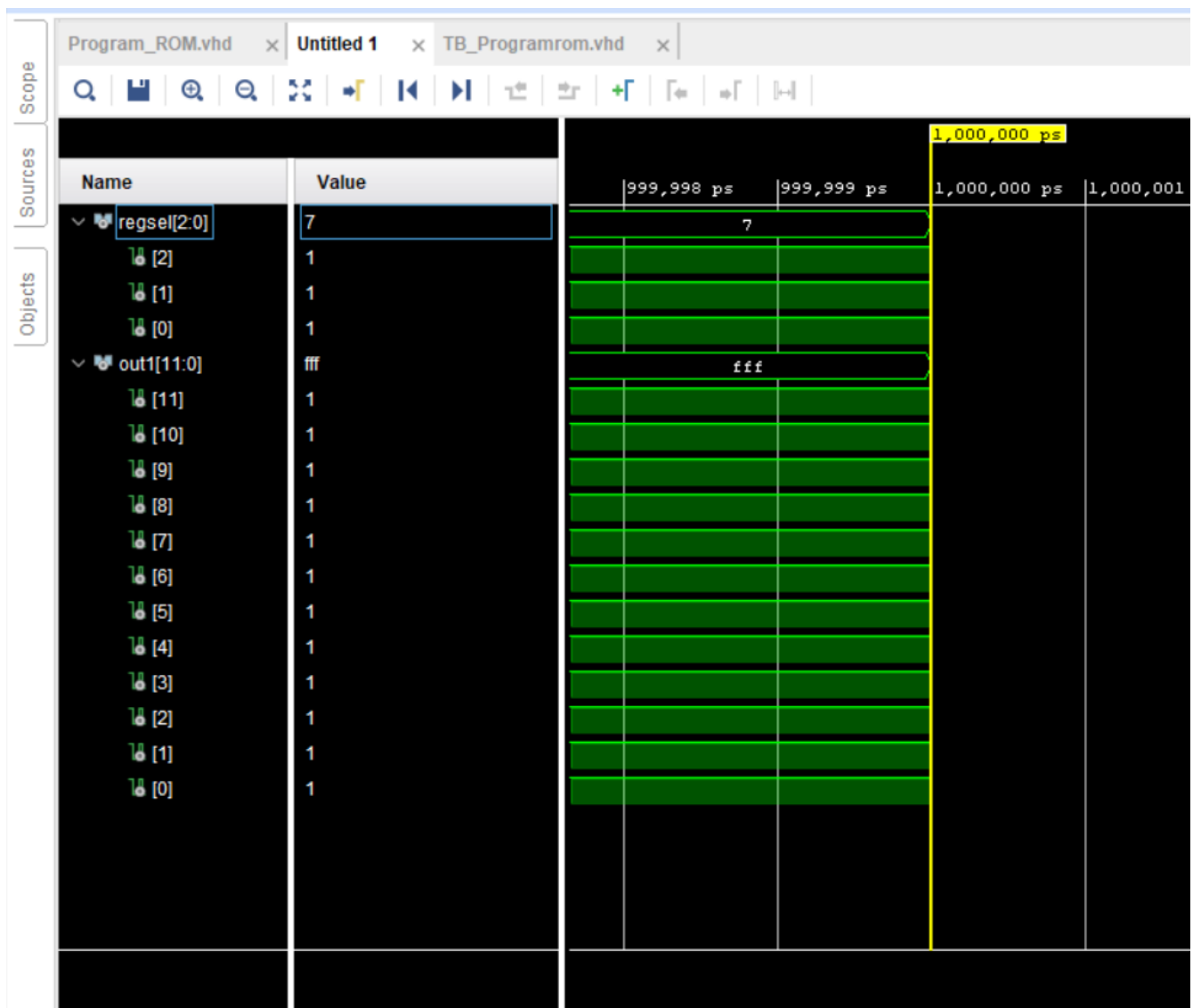

## 4-Bit Add/Sub Unit

### Code

entity fourbitaddsubunit is

```
Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
      B : in STD_LOGIC_VECTOR (3 downto 0);
      Cal_Control : in STD_LOGIC;
      Overflow : out STD_LOGIC;
      Zero : out STD_LOGIC;
      S : out STD_LOGIC_VECTOR (3 downto 0));
```

end fourbitaddsubunit;

architecture Behavioral of fourbitaddsubunit is

component FA

```
port (
```

```

    A: in std_logic;
    B: in std_logic;
    C_in: in std_logic;
    S: out std_logic;
    C_out: out std_logic);
end component;

SIGNAL B_in, S_out : std_logic_vector(3 downto 0);
SIGNAL FA0_C, FA1_C, FA2_C, FA3_C : std_logic;

begin

B_in(0) <= B(0) XOR Cal_Control;
B_in(1) <= B(1) XOR Cal_Control;
B_in(2) <= B(2) XOR Cal_Control;
B_in(3) <= B(3) XOR Cal_Control;

FA_0 : FA
port map (
    A => A(0),
    B => B_in(0),
    C_in => Cal_Control,
    S => S_out(0),
    C_Out => FA0_C);

FA_1 : FA
port map (
    A => A(1),
    B => B_in(1),
    C_in => FA0_C,
    S => S_out(1),
    C_Out => FA1_C);

FA_2 : FA
port map (
    A => A(2),
    B => B_in(2),
    C_in => FA1_C,
    S => S_out(2),
    C_Out => FA2_C);

FA_3 : FA
port map (
    A => A(3),
    B => B_in(3),
    C_in => FA2_C,
    S => S_out(3),
    C_Out => FA3_C);

```

Overflow <= (FA3\_C XOR FA2\_C);

S(0) <= S\_out(0);

S(1) <= S\_out(1);


S(2) <= S\_out(2);

S(3) <= S\_out(3);


Zero <= not (S\_out(0) or S\_out(1) or S\_out(2) or S\_out(3));

end Behavioral;

## RTL

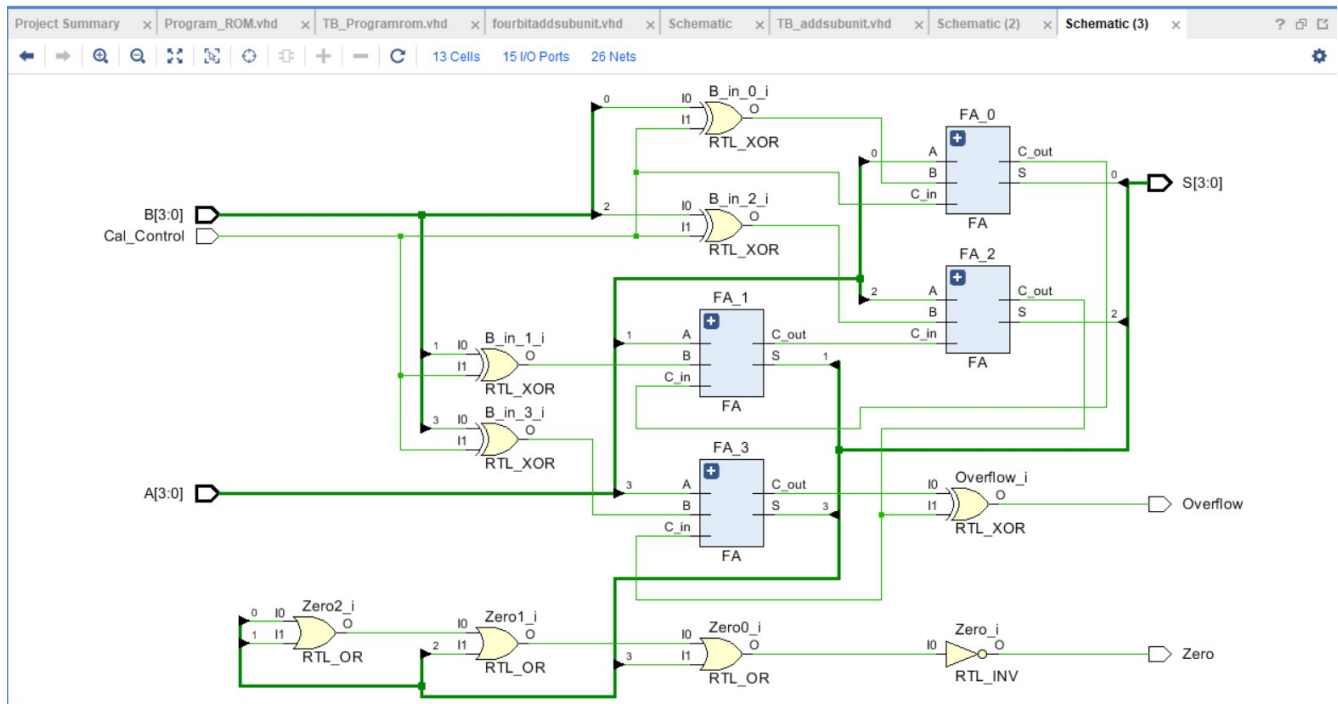

## Synthesized Design

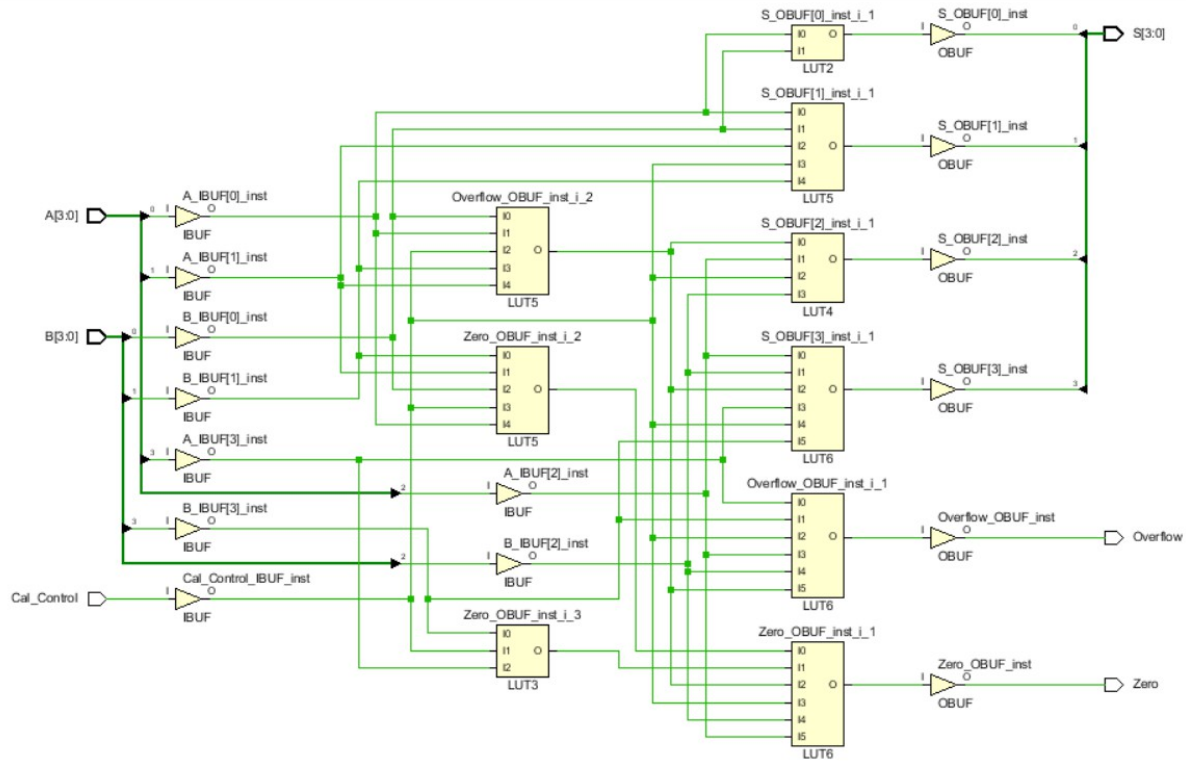

## Simulation\_Code

entity TB\_addsubunit is

-- Port ( );

end TB\_addsubunit;

architecture Behavioral of TB\_addsubunit is

component fourbitaddsubunit is

Port ( A : in STD\_LOGIC\_VECTOR (3 downto 0);

B : in STD\_LOGIC\_VECTOR (3 downto 0);

Cal\_Control : in STD\_LOGIC;

Overflow : out STD\_LOGIC;

Zero : out STD\_LOGIC;

S : out STD\_LOGIC\_VECTOR (3 downto 0));

end component;

signal A : STD\_LOGIC\_VECTOR (3 downto 0);

signal B : STD\_LOGIC\_VECTOR (3 downto 0);

signal Cal\_Control : STD\_LOGIC;

signal Overflow : STD\_LOGIC;

signal Zero : STD\_LOGIC;

signal S : STD\_LOGIC\_VECTOR (3 downto 0);

begin



```

uut : fourbitaddsubunit port map(
    A=>A,
    B=>B,
    Cal_Control => Cal_Control,
    Overflow => Overflow,
    zero => zero,
    s=>s);

```

```

stim_PROC: PROCESS
BEGIN

```

```

A <= "1110";
B <= "1111";
Cal_control <='0';
wait for 100 ns;

```

```

A <= "1011";
B <= "0011";
Cal_control <='0';
wait for 100 ns;

```

```

A <= "1101";
B <= "1011";
Cal_control <='1';
wait for 100 ns;
A <= "1101";
B <= "1011";
Cal_control <='0';
wait for 100 ns;
A <= "1101";
B <= "1001";
Cal_control <='0';
wait for 100 ns;

```

```

A <= "0000";
B <= "0000";
Cal_control <='0';
wait for 100 ns;
A <= "1111";
B <= "1111";
Cal_control <='1';
wait for 100 ns;
A <= "0011";
B <= "0111";
Cal_control <='1';
wait;

```


```

end process;

```

end;

## Behavioral Simulation

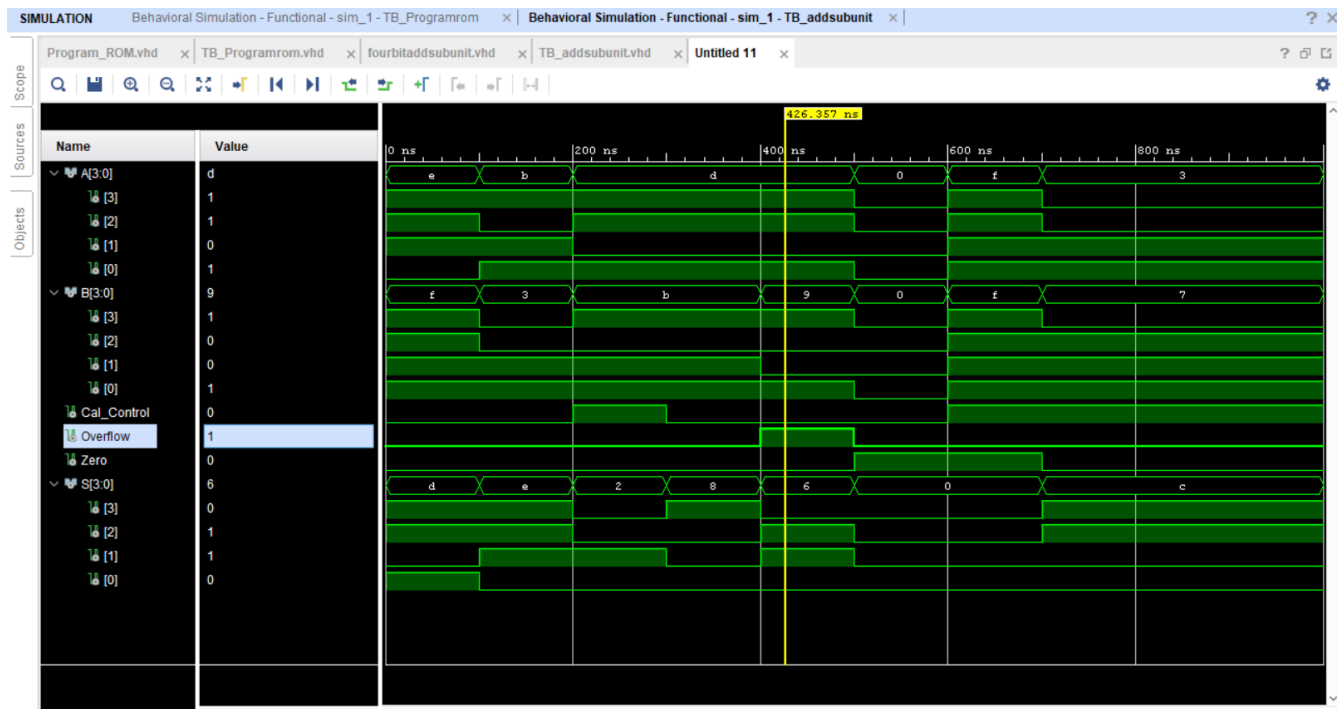

## Decoder 2 to 4

**Code**

```
entity Decoder_2_to_4 is
  Port ( I : in STD_LOGIC_VECTOR (1 downto 0);
        Y : out STD_LOGIC_VECTOR (3 downto 0);
        EN : in STD_LOGIC);
end Decoder_2_to_4;
```

```
architecture Behavioral of Decoder_2_to_4 is
    signal I0_n, I1_n : std_logic;
begin
```

```


I0_n <= not(I(0));
I1_n <= not(I(1));

Y(0) <= (I0_n and I1_n and EN);
Y(1) <= (I(0) and I1_n and EN);
Y(2) <= (I0_n and I(1) and EN);
Y(3) <= (I(0) and I(1) and EN);


```

end Behavioral;

## RTL

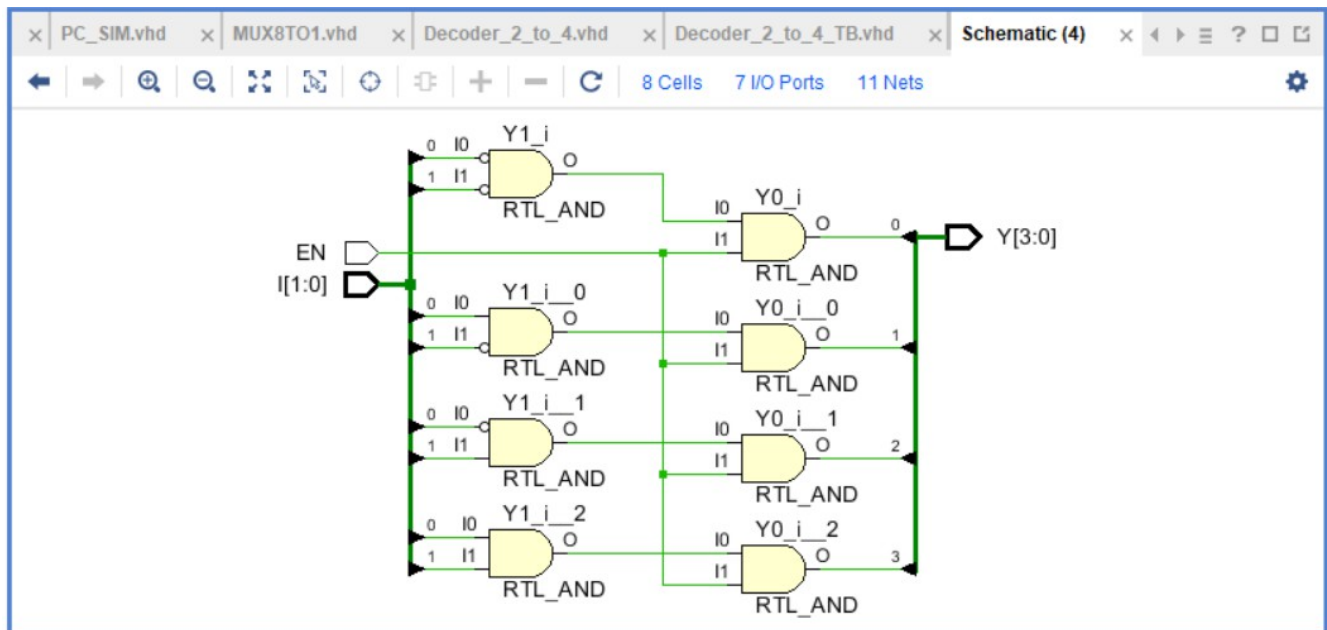

## Synthesized Design

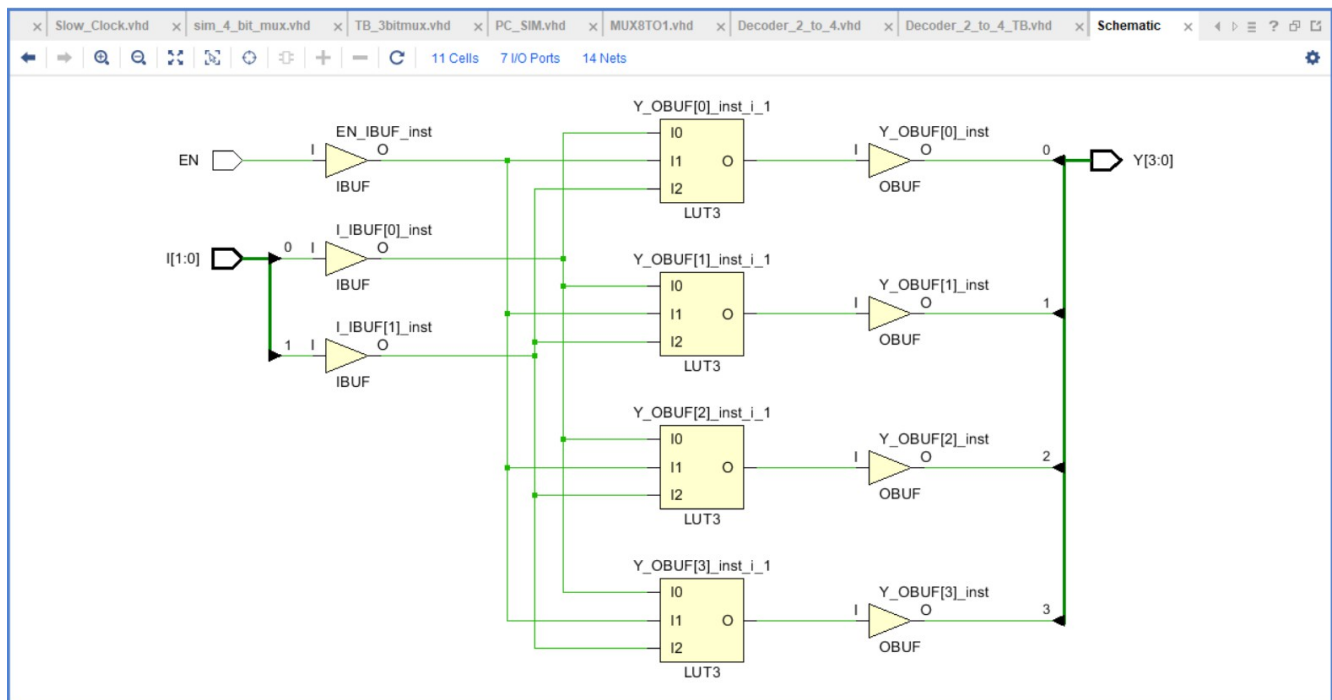

## Simulation Code

```
entity Decoder_2_to_4_TB is
-- Port ();
end Decoder_2_to_4_TB;
```

architecture Behavioral of Decoder\_2\_to\_4\_TB is

```
component Decoder_2_to_4
  port ( I : in STD_logic_vector (1 downto 0);
        EN: in std_logic;
        y: out std_logic_vector (3 downto 0));
end component;

signal I1 :STD_logic_vector (1 downto 0):= (others => '0');
signal EN1 :STD_logic:= '0';


signal y1 :STD_logic_vector (3 downto 0);
begin

uut: Decoder_2_to_4 port map(
  I => I1,
  EN => EN1,
  Y => Y1
);

process
begin
  EN1 <= '1';

  wait for 100 ns;
  I1 <= "00";
  wait for 100 ns;
  I1 <= "01";
  wait for 100 ns;
  I1 <= "10";
  wait for 100 ns;
  I1 <= "11";
  wait;
end process;
end Behavioral;
```

### **Behavioral Simulation**

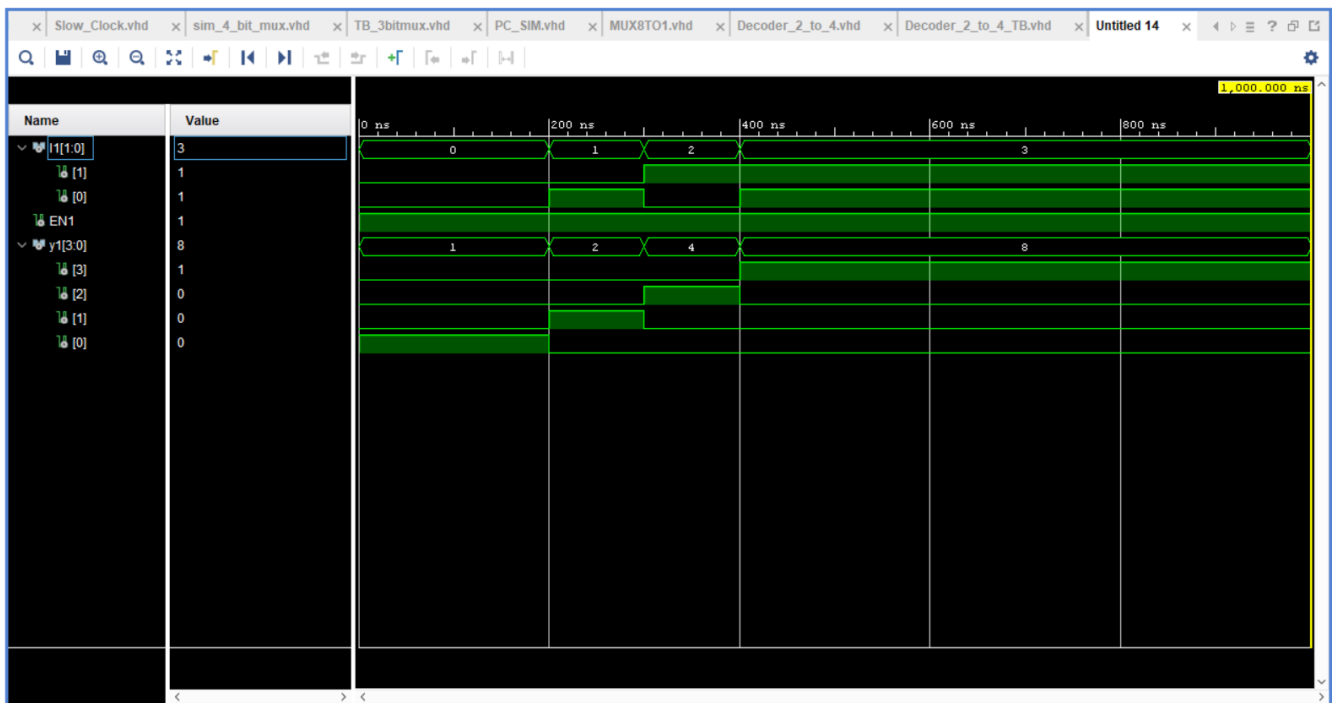

## [Decoder 3 to 8](#)

### Code

```
entity Decoder_3_to_8 is
  Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
        EN : in STD_LOGIC;
        Y : out STD_LOGIC_VECTOR (7 downto 0));
end Decoder_3_to_8;
```

architecture Behavioral of Decoder\_3\_to\_8 is

```
component Decoder_2_to_4
  Port ( I : in STD_LOGIC_VECTOR (1 downto 0);
        EN : in STD_LOGIC;
        Y : out STD_LOGIC_VECTOR (3 downto 0));
end component;
```

```
signal Y0, Y1 : std_logic_vector ( 3 downto 0);
```

```
begin
```

```
Decoder_2_to_4_0:Decoder_2_to_4 port map (
  I (1 downto 0) => I (1 downto 0),
  EN => EN,
  Y (3 downto 0) => Y0 (3 downto 0));
```


```
Decoder_2_to_4_1:Decoder_2_to_4 port map (  
    I (1 downto 0) => I (1 downto 0),  
    EN => EN,  
    Y (3 downto 0) => Y1 (3 downto 0));
```

```
Y(0) <= Y0(0) and (not I(2));  
Y(1) <= Y0(1) and (not I(2));  
Y(2) <= Y0(2) and (not I(2));  
Y(3) <= Y0(3) and (not I(2));
```


```
Y(4) <= Y1(0) and (I(2));  
Y(5) <= Y1(1) and (I(2));  
Y(6) <= Y1(2) and (I(2));  
Y(7) <= Y1(3) and (I(2));
```

```
end Behavioral;
```

**RTL**

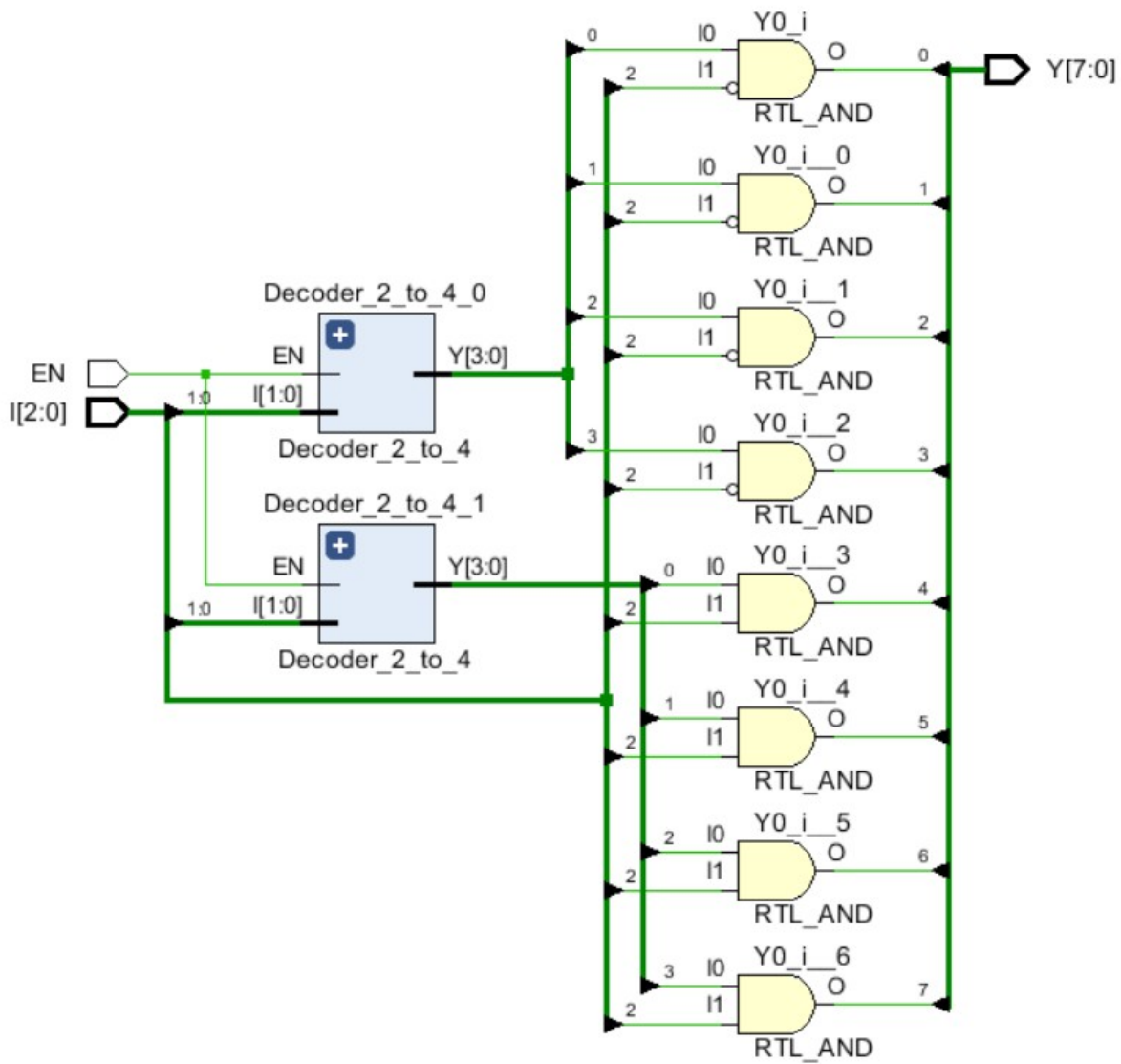

## Synthesized Design

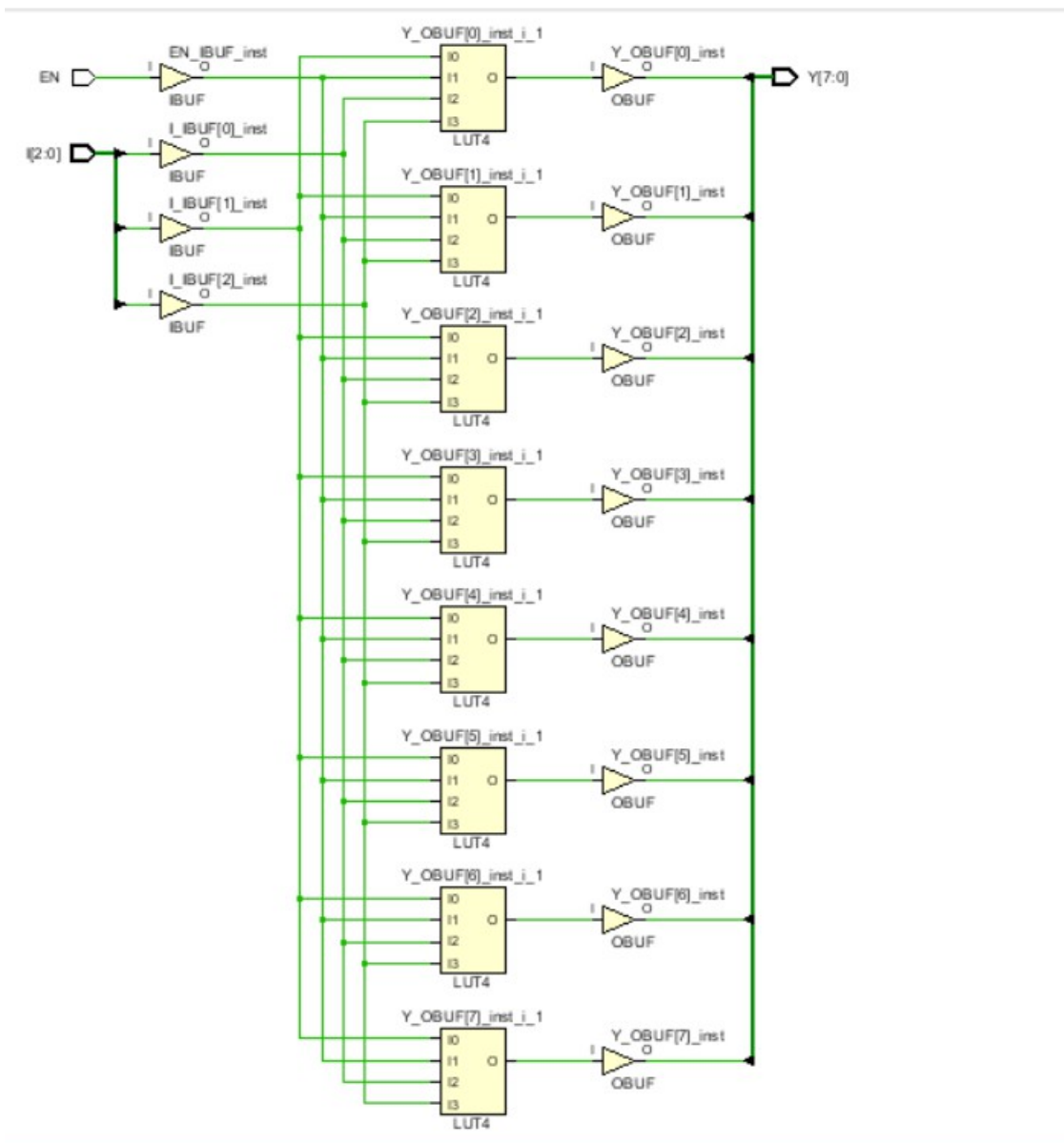

## Simulation\_Code

entity TB\_Decoder\_3\_to\_8 is

-- Port ();

end TB\_Decoder\_3\_to\_8;

architecture Behavioral of TB\_Decoder\_3\_to\_8 is

component Decoder\_3\_to\_8

Port ( I : in STD\_LOGIC\_VECTOR (2 downto 0);

EN : in STD\_LOGIC;

Y : out STD\_LOGIC\_VECTOR (7 downto 0));



```

end component;

signal I : std_logic_vector (2 downto 0);
signal EN : std_logic;
signal Y : std_logic_vector (7 downto 0);

begin


UUT : Decoder_3_to_8 port map (
    I => I,
    EN => EN,
    Y => Y);

sium : process

    begin EN <= '1';
    wait for 100 ns;
    I <= "000";
    wait for 100 ns;
    I <= "001";
    wait for 100 ns;
    I <= "010";
    wait for 100 ns;
    I <= "011";
    wait for 100 ns;
    I <= "100";
    wait for 100 ns;
    I <= "101";
    wait for 100 ns;
    I <= "110";
    wait for 100 ns;
    I <= "111";
    wait;
    end process;
end Behavioral;

```

### **Behavioral Simulation**

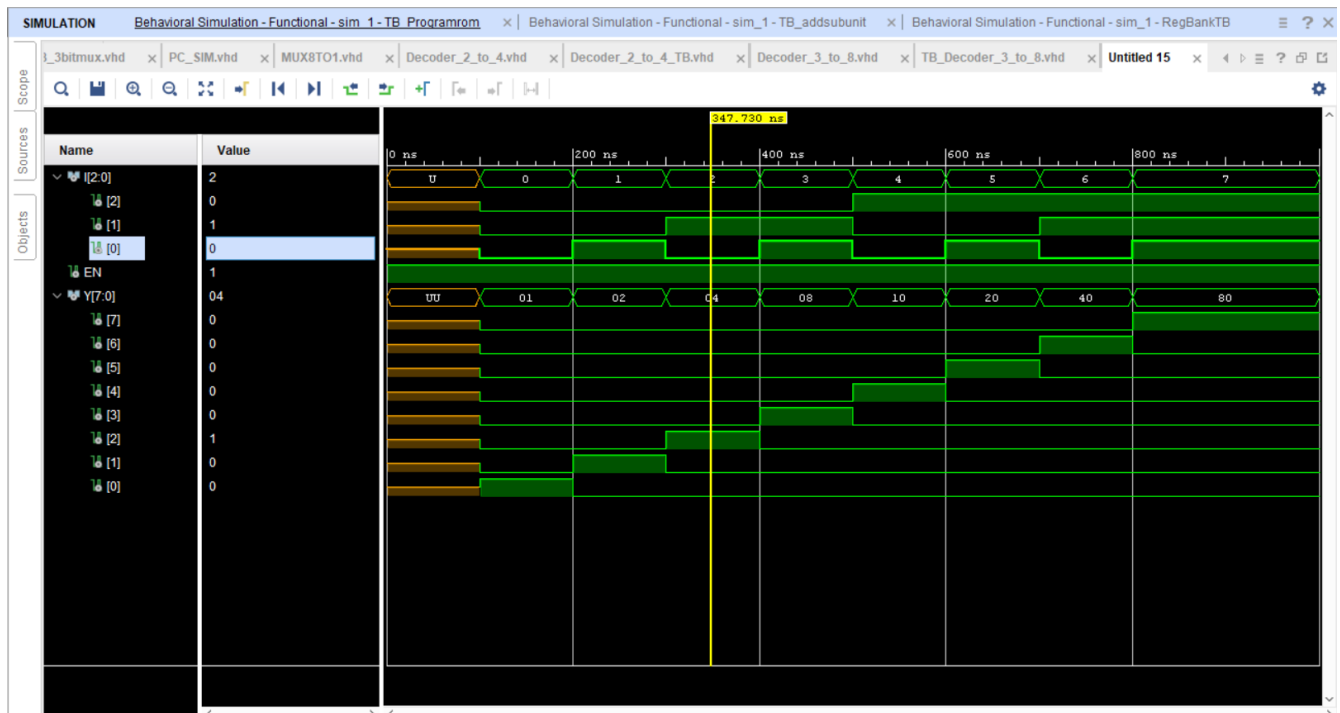

## D\_FF\_WITH\_EN

### Code

```
entity D_FF_WITH_EN is
  Port ( D : in STD_LOGIC;
        En : in STD_LOGIC;
        Res : in STD_LOGIC;
        Clk : in STD_LOGIC;
        Q : out STD_LOGIC;
        Qbar : out STD_LOGIC);
end D_FF_WITH_EN;
```

architecture Behavioral of D\_FF\_WITH\_EN is

```
Component D_FF Port ( D : in STD_LOGIC;
  Res : in STD_LOGIC;
  Clk : in STD_LOGIC;
  Q : out STD_LOGIC;
  Qbar : out STD_LOGIC);
end component;
```

```
signal res0,clk0,d0,en0,not_en0,q0,qbar0,inter0,inter1,inter2:std_logic;
```

```
begin
```

```
D_FF0 : D_FF Port map
  ( D => inter1,
```

```

Res =>res0,
Clk =>clk0,
Q =>q0,
Qbar =>qbar0);

```

```

d0 <= d;
en0 <= en;
res0<=res;
clk0<=clk;

```

```

q<=q0;
qbar<=qbar0;

```

```

inter0<= d0 and en0;

```

```

not_en0<=not en0;
inter2<=not_en0 and q0;

```

```

inter1<=inter2 or inter0;


```

```


end Behavioral;

```

## RTL

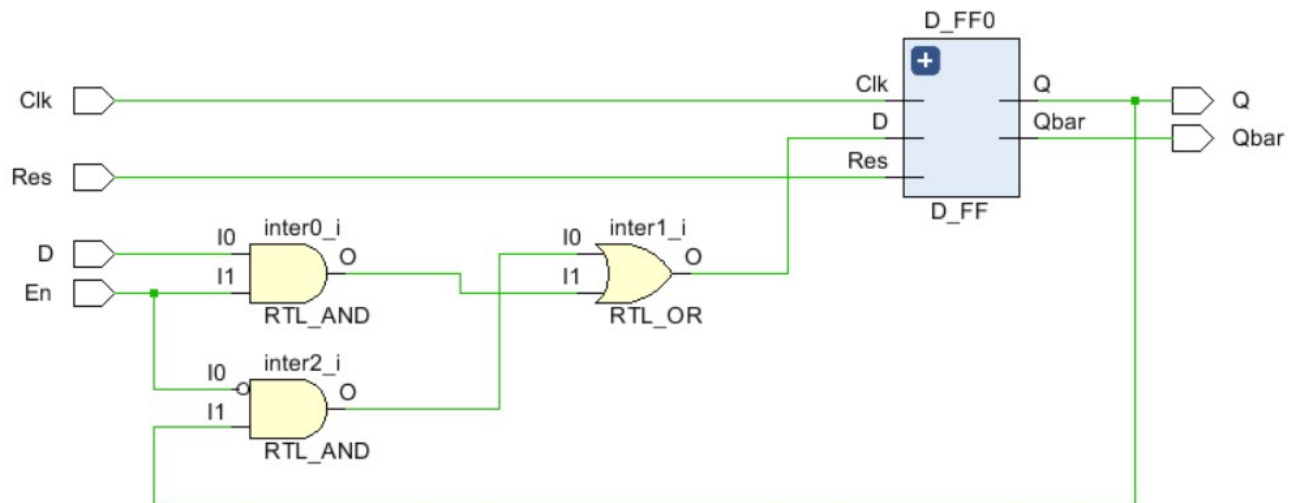

## Synthesized Design

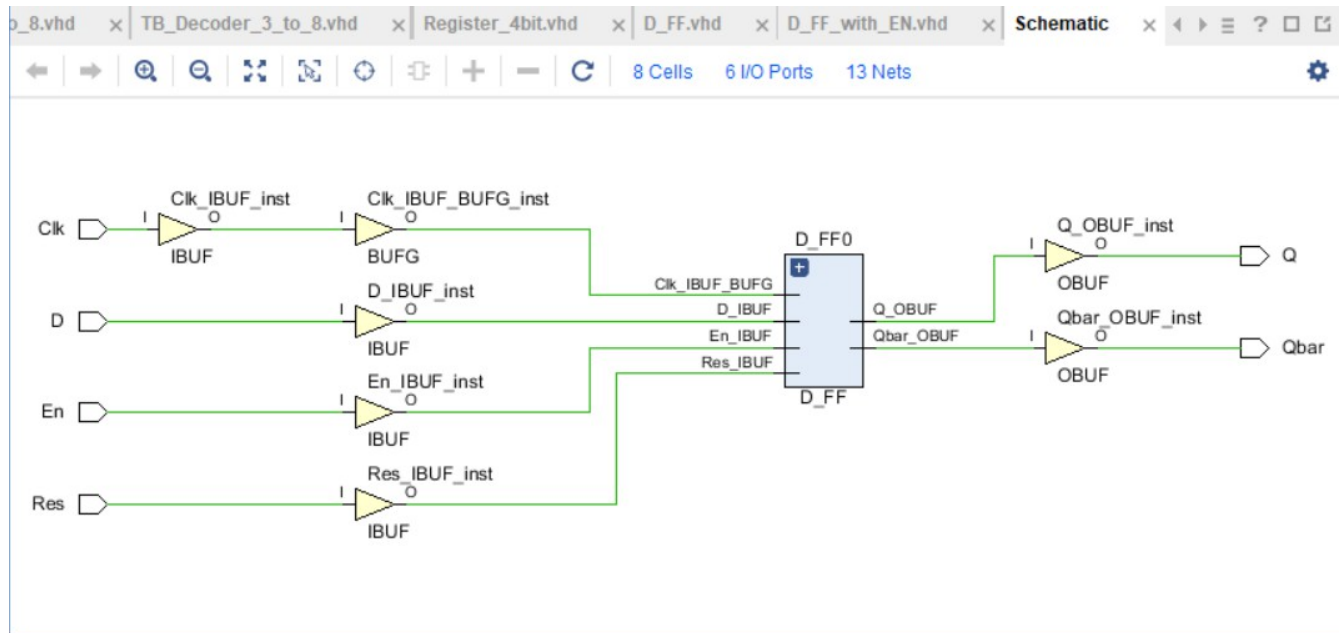

## Register\_4bit

### Code

entity Register\_4bit is

```
Port ( RegIn : in STD_LOGIC_VECTOR (3 downto 0);  
      RegOut : out STD_LOGIC_VECTOR (3 downto 0);  
      Clock : in STD_LOGIC;  
      RegEnable : in STD_LOGIC;  
      RegReset : in STD_LOGIC);
```

end Register\_4bit;

architecture Behavioral of Register\_4bit is

```
component D_FF_WITH_EN Port ( D : in STD_LOGIC;  
  En : in STD_LOGIC;  
  Res : in STD_LOGIC;  
  Clk : in STD_LOGIC;  
  Q : out STD_LOGIC;  
  Qbar : out STD_LOGIC);  
end component;
```

```
signal cout0,cout1,cout2,cout3,cin:std_logic;
```

```
begin
```


```

D_FF_0: D_FF_WITH_EN port map(
    d=> RegIn(0),
    en =>RegEnable,
    res=>RegReset,
    clk=>Clock,
    q=>RegOut(0)
);
D_FF_1: D_FF_WITH_EN port map(
    d=> RegIn(1),
    en =>RegEnable,
    res=>RegReset,
    clk=>Clock,
    q=>RegOut(1)
);
D_FF_2: D_FF_WITH_EN port map(
    d=> RegIn(2),
    en =>RegEnable,
    res=>RegReset,
    clk=>Clock,
    q=>RegOut(2)
);
D_FF_3: D_FF_WITH_EN port map(
    d=> RegIn(3),
    en =>RegEnable,
    res=>RegReset,
    clk=>Clock,
    q=>RegOut(3)
);


```

end Behavioral;

**RTL**

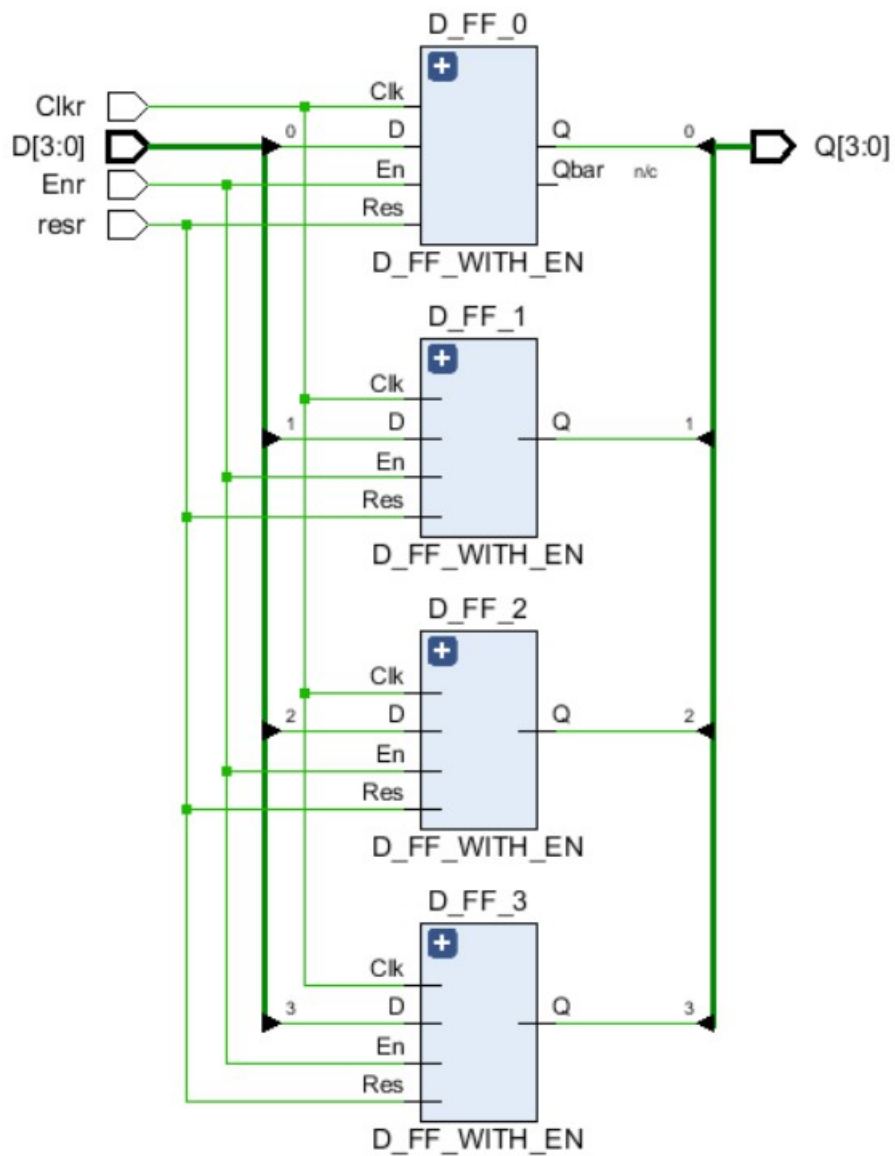

**Synthesized Design**

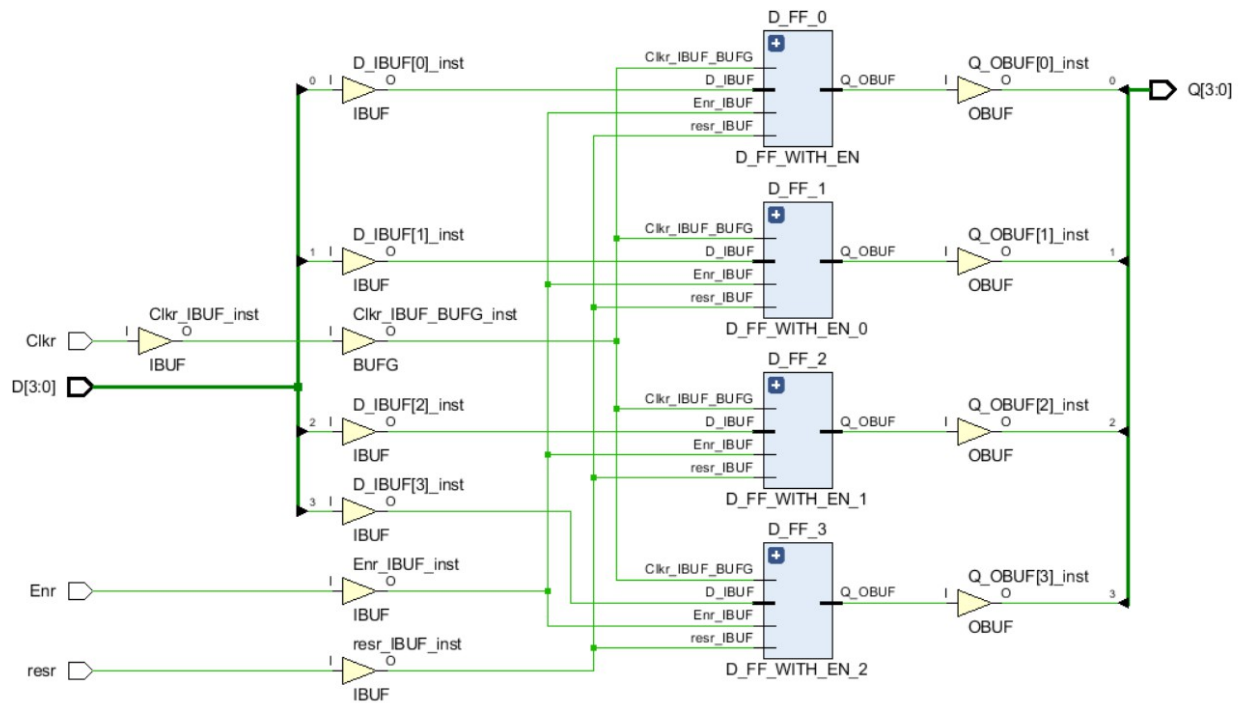

## Register Bank

### Code

entity RegisterBank is

```
Port ( RegisterBank_In : in STD_LOGIC_VECTOR (3 downto 0) ;
      RegisterBank_Reset : in STD_LOGIC;
      Register_Select : in STD_LOGIC_VECTOR (2 downto 0);
      Clock : in STD_LOGIC;
      Register0_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register1_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register2_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register3_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register4_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register5_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register6_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register7_Out : out STD_LOGIC_VECTOR (3 downto 0));
```

end RegisterBank;

architecture Behavioral of RegisterBank is

component Register\_4bit is

```
Port ( RegIn : in STD_LOGIC_VECTOR (3 downto 0);
      RegOut : out STD_LOGIC_VECTOR (3 downto 0);
      Clock : in STD_LOGIC;
      RegEnable : in STD_LOGIC;
      RegReset : in STD_LOGIC);
```

end component;

```

component Decoder_3_to_8 is
  Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
        EN : in STD_LOGIC;
        Y : out STD_LOGIC_VECTOR (7 downto 0));
end component;

Signal Active: std_logic;
Signal RegisterSelector: std_logic_vector (7 downto 0);

begin

Active <= '1';

Decoder : Decoder_3_to_8
port map(
  I => Register_Select,
  EN => Active,
  Y => RegisterSelector);

Reg0 : Register_4bit
port map(
  RegIn => RegisterBank_In,
  RegOut => Register0_Out,
  RegReset => RegisterBank_Reset,
  RegEnable => RegisterSelector(0),
  Clock => Clock);

Reg1 : Register_4bit
port map(
  RegIn => RegisterBank_In,
  RegOut => Register1_Out,
  RegReset => RegisterBank_Reset,
  RegEnable => RegisterSelector(1),
  Clock => Clock);

Reg2 : Register_4bit
port map(
  RegIn => RegisterBank_In,
  RegOut => Register2_Out,
  RegReset => RegisterBank_Reset,
  RegEnable => RegisterSelector(2),
  Clock => Clock);

Reg3 : Register_4bit
port map(
  RegIn => RegisterBank_In,
  RegOut => Register3_Out,
  RegReset => RegisterBank_Reset,

```



```
RegEnable => RegisterSelector(3),  
Clock => Clock);
```

```
Reg4 : Register_4bit
```

```
port map(  
  RegIn => RegisterBank_In,  
  RegOut => Register4_Out,  
  RegReset => RegisterBank_Reset,  
  RegEnable => RegisterSelector(4),  
  Clock => Clock);
```

```
Reg5 : Register_4bit
```

```
port map(  
  RegIn => RegisterBank_In,  
  RegOut => Register5_Out,  
  RegReset => RegisterBank_Reset,  
  RegEnable => RegisterSelector(5),  
  Clock => Clock);
```

```
Reg6 : Register_4bit
```


```
port map(  
  RegIn => RegisterBank_In,  
  RegOut => Register6_Out,  
  RegReset => RegisterBank_Reset,  
  RegEnable => RegisterSelector(6),  
  Clock => Clock);
```

```
Reg7 : Register_4bit
```


```
port map(  
  RegIn => RegisterBank_In,  
  RegOut => Register7_Out,  
  RegReset => RegisterBank_Reset,  
  RegEnable => RegisterSelector(7),  
  Clock => Clock);
```

```
end Behavioral;
```

**RTL**

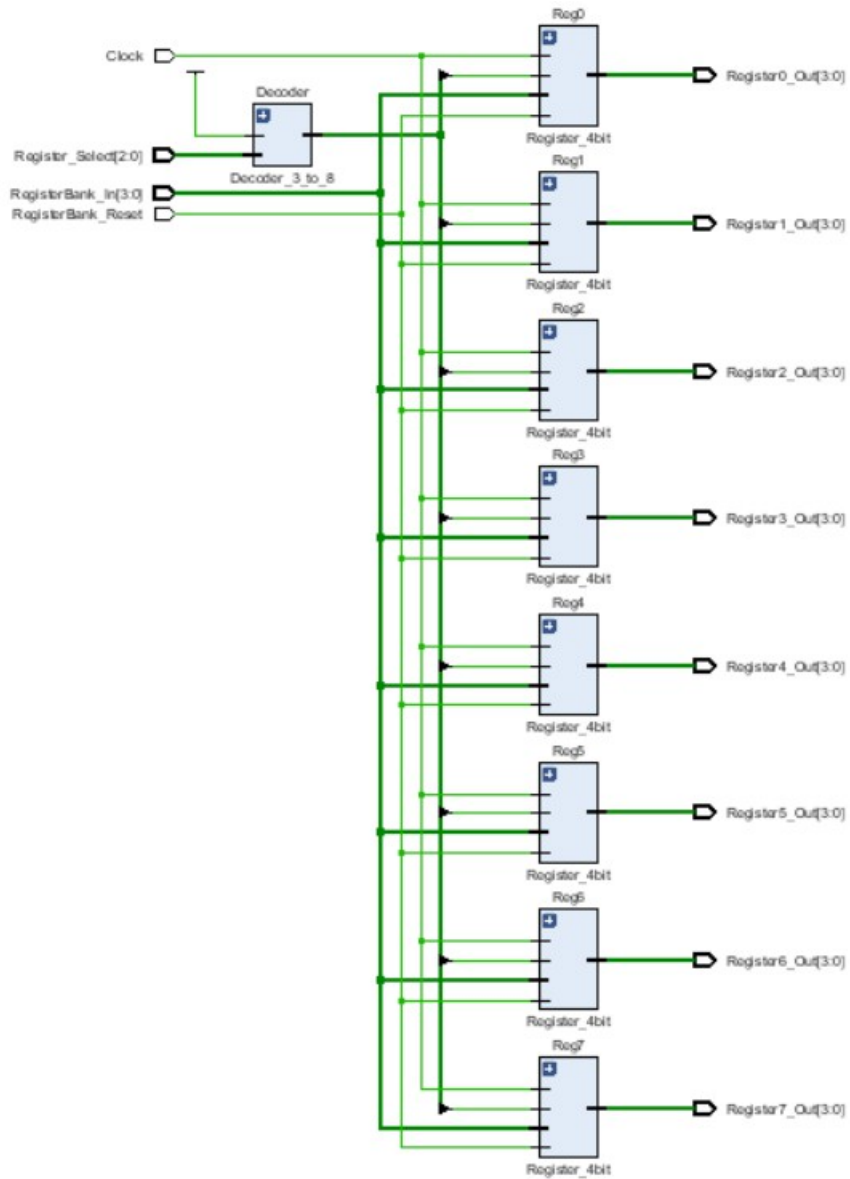

## Synthesized Design

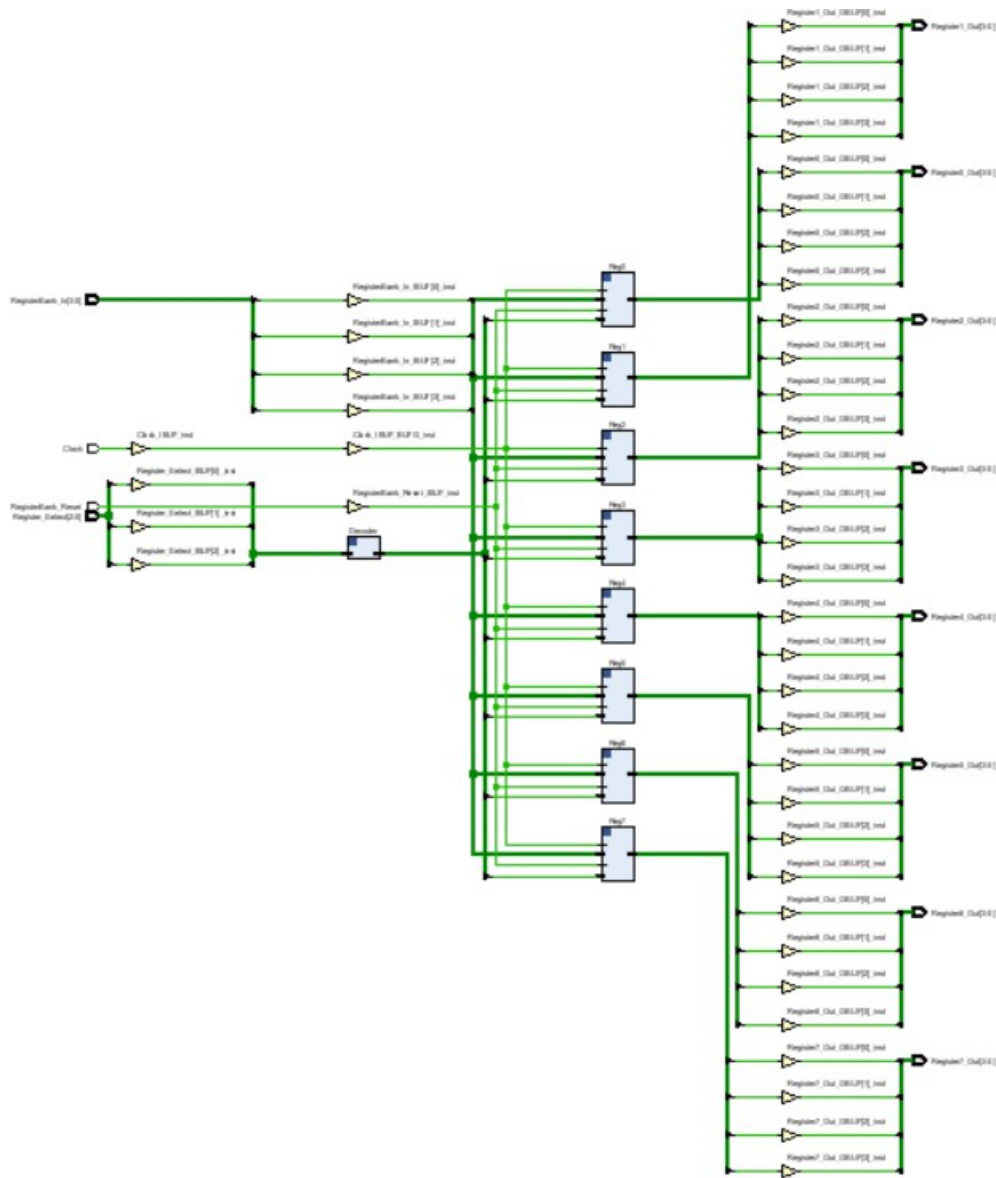

## Simulation\_Code

entity RegBankTB is  
 -- Port ();  
end RegBankTB;

architecture Behavioral of RegBankTB is  
 component RegisterBank is

Port ( RegisterBank\_In : in STD\_LOGIC\_VECTOR (3 downto 0);  
 RegisterBank\_Reset : in STD\_LOGIC;  
 Register\_Select : in STD\_LOGIC\_VECTOR (2 downto 0);  
 Clock : in STD\_LOGIC;  
 Register0\_Out : out STD\_LOGIC\_VECTOR (3 downto 0);  
 Register1\_Out : out STD\_LOGIC\_VECTOR (3 downto 0);  
 Register2\_Out : out STD\_LOGIC\_VECTOR (3 downto 0);

```

    Register3_Out : out STD_LOGIC_VECTOR (3 downto 0);
    Register4_Out : out STD_LOGIC_VECTOR (3 downto 0);
    Register5_Out : out STD_LOGIC_VECTOR (3 downto 0);
    Register6_Out : out STD_LOGIC_VECTOR (3 downto 0);
    Register7_Out : out STD_LOGIC_VECTOR (3 downto 0));
end component;

    signal RegisterBank_In : STD_LOGIC_VECTOR (3 downto 0);
    signal RegisterBank_Reset : STD_LOGIC;
    signal Register_Select : STD_LOGIC_VECTOR (2 downto 0);
    signal Clock : STD_LOGIC;
    signal Register0_Out : STD_LOGIC_VECTOR (3 downto 0);
    signal Register1_Out : STD_LOGIC_VECTOR (3 downto 0);
    signal Register2_Out : STD_LOGIC_VECTOR (3 downto 0);
    signal Register3_Out : STD_LOGIC_VECTOR (3 downto 0);
    signal Register4_Out : STD_LOGIC_VECTOR (3 downto 0);
    signal Register5_Out : STD_LOGIC_VECTOR (3 downto 0);
    signal Register6_Out : STD_LOGIC_VECTOR (3 downto 0);
    signal Register7_Out : STD_LOGIC_VECTOR (3 downto 0);
    constant clk_period : time := 10 ns;

begin

uut : registerbank port map(
    RegisterBank_In => RegisterBank_In,
    RegisterBank_Reset => RegisterBank_Reset,
    Register_Select => Register_Select,
    Clock => Clock,
    Register0_Out => Register0_Out,
    Register1_Out => Register1_Out,
    Register2_Out => Register2_Out,
    Register3_Out => Register3_Out,
    Register4_Out => Register4_Out,
    Register5_Out => Register5_Out,
    Register6_Out => Register6_Out,
    Register7_Out => Register7_Out
);

clk_process : process
    begin
        Clock <= '0';
        wait for clk_period/2;
        Clock <= '1';
        wait for clk_period/2;
    end process;

stim_PROC: PROCESS
BEGIN

    RegisterBank_In <= "1111";

```

```

RegisterBank_Reset<='0';
Register_Select<="000";
wait for 100 ns;
RegisterBank_In<="1111";
RegisterBank_Reset<='0';
Register_Select<="001";
wait for 100 ns;
RegisterBank_In<="1111";
RegisterBank_Reset<='0';
Register_Select<="010";
wait for 100 ns;
RegisterBank_In<="1111";
RegisterBank_Reset<='0';
Register_Select<="011";
wait for 100 ns;
RegisterBank_In<="1111";
RegisterBank_Reset<='0';
Register_Select<="100";
wait for 100 ns;
RegisterBank_In<="1111";
RegisterBank_Reset<='0';
Register_Select<="101";
wait for 100 ns;
RegisterBank_In<="1111";
RegisterBank_Reset<='0';
Register_Select<="110";
wait for 100 ns;
RegisterBank_In<="1111";
RegisterBank_Reset<='0';
Register_Select<="111";
wait for 100 ns;

```

```

RegisterBank_In<="1111";
RegisterBank_Reset<='1';
Register_Select<="000";
wait for 100 ns;


```

```

end process;
end;

```

### **Behavioral Simulation**

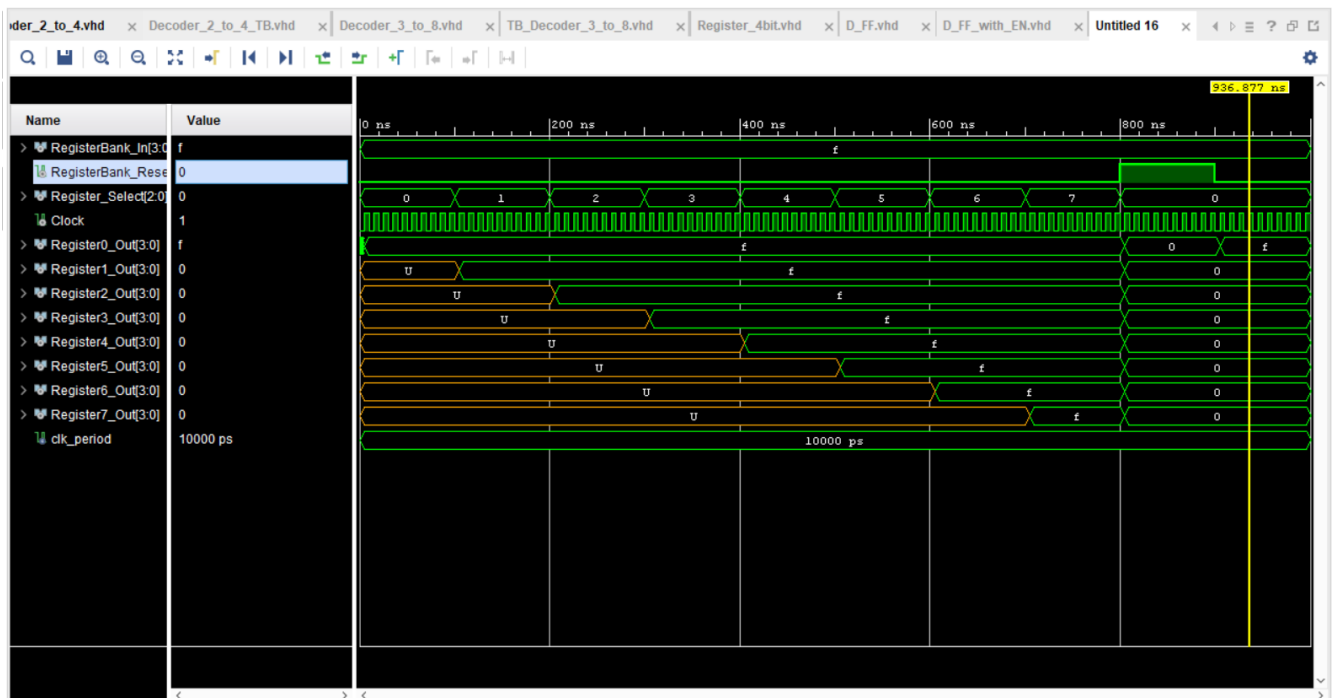

## Instruction Decoder

### Code

entity Instruction\_Decoder is

```
Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0);
      RegisterCheckkJump : in STD_LOGIC_VECTOR (3 downto 0);
      RegisterEnable : out STD_LOGIC_VECTOR (2 downto 0);
      LoadSelect : out STD_LOGIC;
      ImmValue : out STD_LOGIC_VECTOR (3 downto 0);
      RegisterSelect_1 : out STD_LOGIC_VECTOR (2 downto 0);
      RegisterSelect_2 : out STD_LOGIC_VECTOR (2 downto 0);
      AddSub_Select : out STD_LOGIC;
      JumpFlag : out STD_LOGIC;
      JumpAdder : out STD_LOGIC_VECTOR (2 downto 0));
```

end Instruction\_Decoder;

architecture Behavioral of Instruction\_Decoder is

component Decoder\_2\_to\_4

```
port(
  I: in std_logic_vector(1 downto 0);
  En: in std_logic;
  Y: out std_logic_vector(3 downto 0));
end component;
```

Signal add, neg, mov, jzr : std\_logic;

```

Signal var1 : std_logic;
signal reg1sel,reg2sel : STD_LOGIC_VECTOR (2 downto 0);

begin

Decoder_2_to_4_0 : Decoder_2_to_4
  port map (
    I(0) => Instruction(10),
    I(1) => Instruction(11),
    EN => '1',
    Y(0)=> add,
    Y(1) => neg,
    Y(2) => mov,
    Y(3) => jzr);

LoadSelect <= mov;
AddSub_Select <= neg;
JumpFlag <=jzr and ((RegisterCheckkJump(0) or RegisterCheckkJump(1) or
RegisterCheckkJump(2)));
JumpAdder <= Instruction (2 downto 0);

var1 <= add or neg or mov;
RegisterEnable(0) <= var1 and Instruction(7);
RegisterEnable(1) <= var1 and Instruction(8);
RegisterEnable(2) <= var1 and Instruction(9);
ImmValue <= Instruction (3 downto 0);

reg1sel(0) <=((Instruction (7))and(not neg));
reg1sel(1) <=((Instruction (8))and(not neg));
reg1sel(2) <=((Instruction (9))and(not neg));


reg2sel(2) <=((Instruction (6))and(not neg)) or ((Instruction (9))and(neg));
reg2sel(1) <=((Instruction (5))and(not neg)) or ((Instruction (8))and(neg));
reg2sel(0) <=((Instruction (4))and(not neg)) or ((Instruction (7))and(neg));

RegisterSelect_1 <= reg1sel;
RegisterSelect_2 <= reg2sel;

end Behavioral;


```

## **RTL**

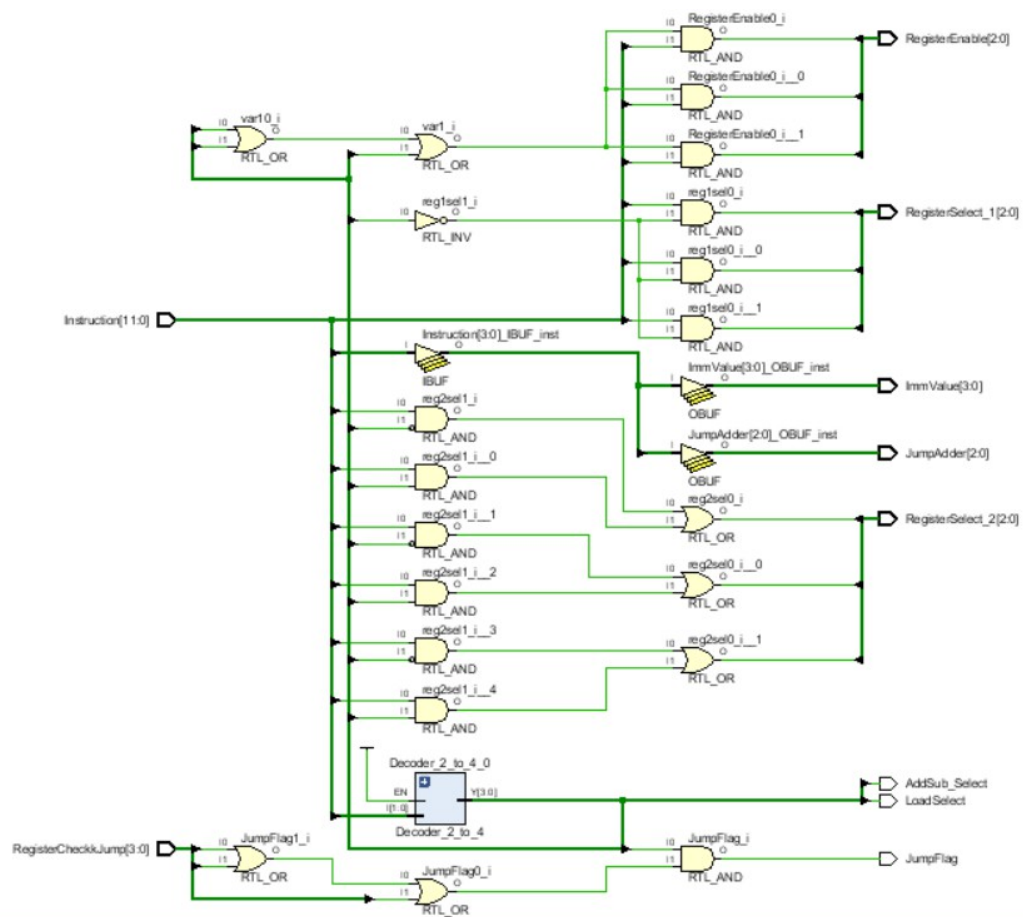

## Synthesized Design



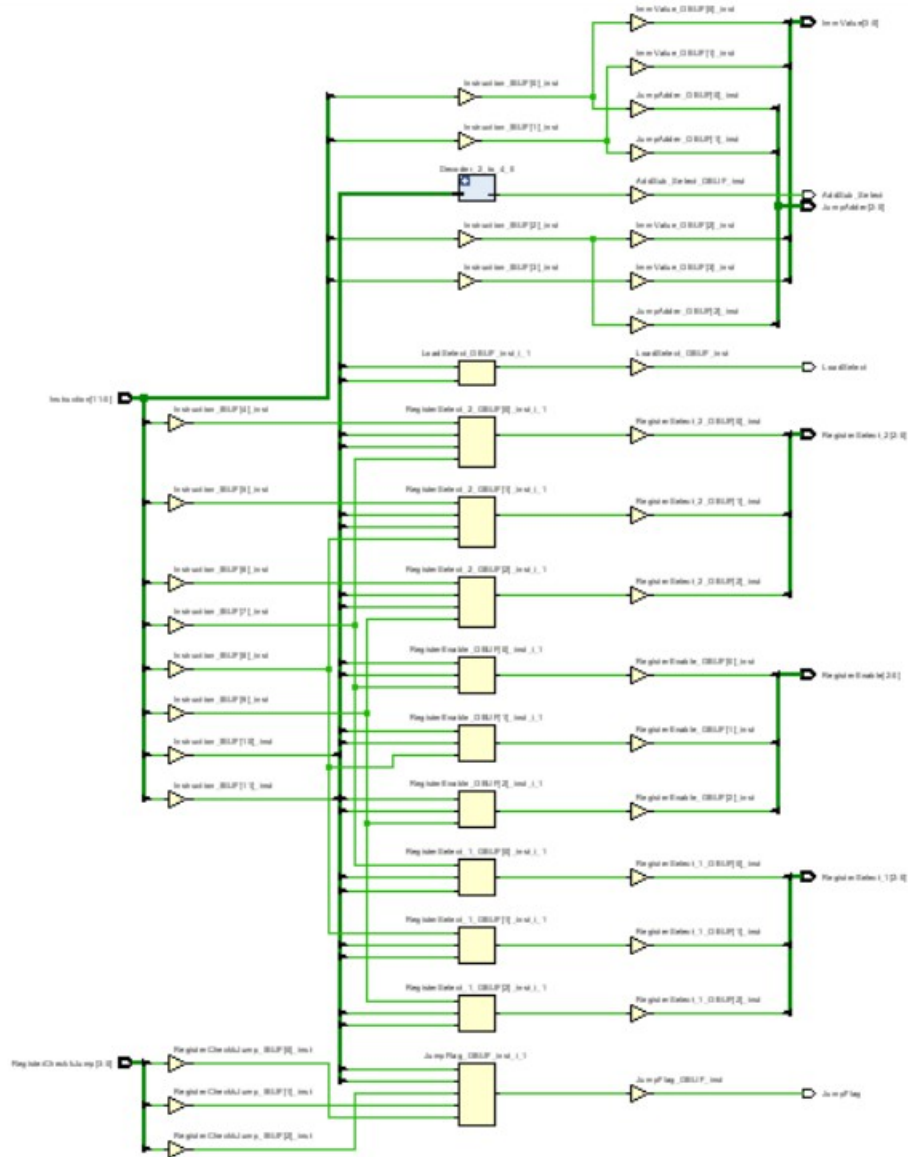

## way2bit4mux

### Code

entity way2bit4mux is

Port ( loadsel : STD\_LOGIC;

load : in STD\_LOGIC\_VECTOR (3 downto 0);

defaultval : in STD\_LOGIC\_VECTOR (3 downto 0);

outval : out STD\_LOGIC\_VECTOR (3 downto 0)

);

end way2bit4mux;


architecture Behavioral of way2bit4mux is

begin

```
outval(0) <= (defaultval(0)and (not loadsel)) or (load(0) and loadsel);  
outval(1) <= (defaultval(1)and (not loadsel)) or (load(1) and loadsel);  
outval(2) <= (defaultval(2)and (not loadsel)) or (load(2) and loadsel);  
outval(3) <= (defaultval(3)and (not loadsel)) or (load(3) and loadsel);
```

end Behavioral;

## RTL

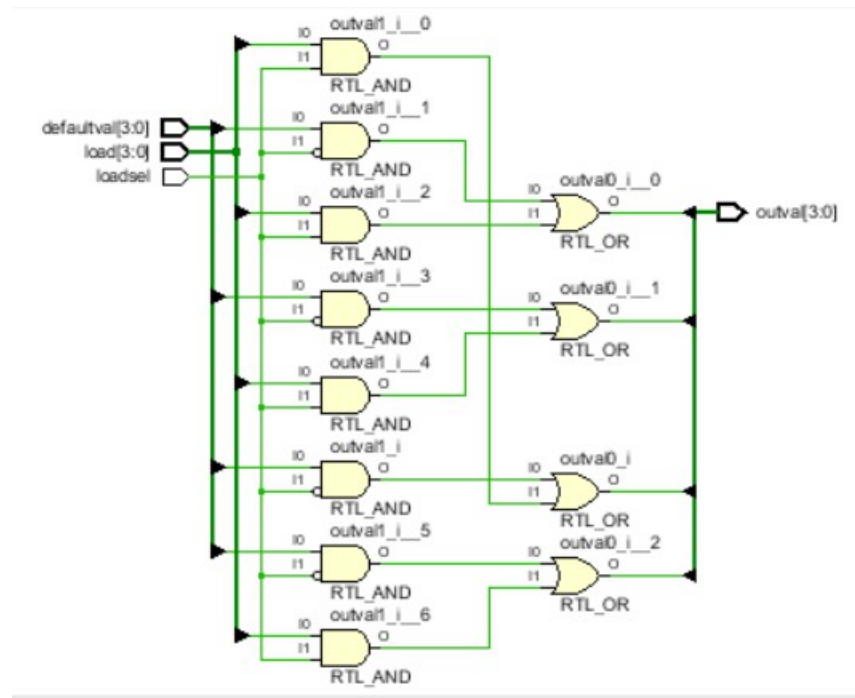

## Micro Processor

### Code

```
entity Micro_Processor is  
  Port ( Clockinn : in STD_LOGIC;  
        Reset : in STD_LOGIC;  
        Overflow : out STD_LOGIC;  
        Zero : out STD_LOGIC;  
        To_Leds : out STD_LOGIC_VECTOR (3 downto 0);  
        PCVAL : out STD_LOGIC_VECTOR (2 downto 0));  
  
end Micro_Processor;
```

architecture Behavioral of Micro\_Processor is

component PROGRAM\_COUNTER

```
Port ( TOIN : in STD_LOGIC_VECTOR (2 downto 0);
      TOOOUT : out STD_LOGIC_VECTOR (2 downto 0);
      CLK : in STD_LOGIC;
      RES : in STD_LOGIC);
```

end component;

component way2bit3mux

```
Port ( jumpflag : in STD_LOGIC;
      addresstojump : in STD_LOGIC_VECTOR (2 downto 0);
      default1 : in STD_LOGIC_VECTOR (2 downto 0);
      out1 : out STD_LOGIC_VECTOR (2 downto 0));
```

end component;

component bit\_3\_adder

```
Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
      S : out STD_LOGIC_VECTOR (2 downto 0)
      );
```

end component;

component program\_rom is

```
Port ( regsel : in STD_LOGIC_VECTOR (2 downto 0);
      out1 : out STD_LOGIC_VECTOR (11 downto 0));
```

end component;

component Instruction\_Decoder is

```
Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0);
      RegisterCheckkJump : in STD_LOGIC_VECTOR (3 downto 0);
      RegisterEnable : out STD_LOGIC_VECTOR (2 downto 0);
      LoadSelect : out STD_LOGIC;
      ImmValue : out STD_LOGIC_VECTOR (3 downto 0);
      RegisterSelect_1 : out STD_LOGIC_VECTOR (2 downto 0);
      RegisterSelect_2 : out STD_LOGIC_VECTOR (2 downto 0);
      AddSub_Select : out STD_LOGIC;
      JumpFlag : out STD_LOGIC;
      JumpAdder : out STD_LOGIC_VECTOR (2 downto 0));
```

end component;

component way2bit4mux is

```
Port ( loadsel : STD_LOGIC;
      load : in STD_LOGIC_VECTOR (3 downto 0);
      defaultval : in STD_LOGIC_VECTOR (3 downto 0);
      outval : out STD_LOGIC_VECTOR (3 downto 0)
      );
```

end component;

component Slow\_Clock is

```
Port ( Clk_in : in STD_LOGIC;
      Clk_out : out STD_LOGIC);
```

end component;

component RegisterBank is

```

Port ( RegisterBank_In : in STD_LOGIC_VECTOR (3 downto 0) ;
      RegisterBank_Reset : in STD_LOGIC;
      Register_Select : in STD_LOGIC_VECTOR (2 downto 0);
      Clock : in STD_LOGIC;
      Register0_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register1_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register2_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register3_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register4_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register5_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register6_Out : out STD_LOGIC_VECTOR (3 downto 0);
      Register7_Out : out STD_LOGIC_VECTOR (3 downto 0));
end component;
component way8bit4mux is
Port ( regsel : in STD_LOGIC_VECTOR (2 downto 0);
      reg0 : in STD_LOGIC_VECTOR (3 downto 0);
      reg1 : in STD_LOGIC_VECTOR (3 downto 0);
      reg2 : in STD_LOGIC_VECTOR (3 downto 0);
      reg3 : in STD_LOGIC_VECTOR (3 downto 0);
      reg4 : in STD_LOGIC_VECTOR (3 downto 0);
      reg5 : in STD_LOGIC_VECTOR (3 downto 0);
      reg6 : in STD_LOGIC_VECTOR (3 downto 0);
      reg7 : in STD_LOGIC_VECTOR (3 downto 0);
      out1 : out STD_LOGIC_VECTOR (3 downto 0));
end component;

component fourbitaddsubunit is
Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
      B : in STD_LOGIC_VECTOR (3 downto 0);
      Cal_Control : in STD_LOGIC;
      Overflow : out STD_LOGIC;
      Zero : out STD_LOGIC;
      S : out STD_LOGIC_VECTOR (3 downto 0));
end component;

signal signal6,newsig,signalid2,signalid6,cclk,rres: STD_LOGIC;
signal signal1,signal2,signal3,signal4,signal5,signal32,signalid1,signalid4,signalid5 :
STD_LOGIC_VECTOR (2 downto 0);
signal signal7 : STD_LOGIC_VECTOR (11 downto 0);
signal signalid3,signal8,signal9,signalid7 : STD_LOGIC_VECTOR (3 downto 0);
signal rbout0,rbout1,rbout2,rbout3,rbout4,rbout5,rbout6,rbout7,signal10,signal11 :
STD_LOGIC_VECTOR (3 downto 0);

begin

```

PROGRAM\_COUNTER0 : PROGRAM\_COUNTER PORT MAP (

```

    TOIN =>signal1 ,
    TOOOUT => signal32,
    CLK => cclk,
    res =>rres );
way2bit3mux0 : way2bit3mux Port map (
    jumpflag =>signal6,
    addresstojump =>signal5,
    default1 =>signal4,
    out1 =>signal1);
bit_3_adder0 : bit_3_adder Port map (
    A =>signal2,
    S =>signal4);
programrom0 : program_rom Port map (
    regsel =>signal3,
    out1 =>signal7 );
instruction_decoder0 : Instruction_Decoder Port map (
    Instruction =>signal7,
    RegisterCheckkJump =>signalid7,
    RegisterEnable =>signalid1,
    LoadSelect =>signalid2,
    ImmValue =>signalid3,
    RegisterSelect_1=>signalid4,
    RegisterSelect_2 =>signalid5,
    AddSub_Select =>signalid6,
    JumpFlag =>signal6,
    JumpAdder =>signal5);

way2bit4mux0 : way2bit4mux Port map (
    loadsel =>signalid2,
    load =>signalid3,
    defaultval =>signal9,
    outval =>signal8
);
slow_clock0 : Slow_Clock Port map (
    Clk_in =>Clockinn,
    Clk_out=>cclk);

RegisterBank0 : RegisterBank Port map (
    RegisterBank_In=>signal8,
    RegisterBank_Reset =>rres,
    Register_Select =>signalid1,
    Clock =>cclk,
    Register0_Out =>rbout0,
    Register1_Out =>rbout1,
    Register2_Out =>rbout2,
    Register3_Out =>rbout3,
    Register4_Out =>rbout4,
    Register5_Out =>rbout5,
    Register6_Out =>rbout6,

```

```
Register7_Out =>rbout7);
```

```
way8bit4mux0 : way8bit4mux Port map (
```

```
    regsel =>signalid4,
```

```
    reg0 =>rbout0,
```

```
    reg1 =>rbout1,
```

```
    reg2 =>rbout2,
```

```
    reg3 =>rbout3,
```

```
    reg4 =>rbout4,
```

```
    reg5 =>rbout5,
```

```
    reg6 =>rbout6,
```

```
    reg7 =>rbout7,
```

```
    out1 =>signal10);
```

```
way8bit4mux1 : way8bit4mux Port map (
```

```
    regsel =>signalid5,
```

```
    reg0 =>rbout0,
```

```
    reg1 =>rbout1,
```

```
    reg2 =>rbout2,
```

```
    reg3 =>rbout3,
```

```
    reg4 =>rbout4,
```

```
    reg5 =>rbout5,
```

```
    reg6 =>rbout6,
```

```
    reg7 =>rbout7,
```

```
    out1 =>signal11);
```

```
fourbitaddsubunit0 : fourbitaddsubunit Port map (
```

```
    A =>signal10,
```

```
    B =>signal11,
```

```
    Cal_Control =>signalid6,
```

```
    Overflow =>overflow,
```

```
    Zero =>zero,
```

```
    S =>signal9);
```

```
signalid7<=signal10;
```

```
To_Leds(0)<=rbout7(0);
```

```
To_Leds(1)<=rbout7(1);
```

```
To_Leds(2)<=rbout7(2);
```

```
To_Leds(3)<=rbout7(3);
```

```
rres <=reset;
```

```
signal3 <= signal32;
```


```
signal2 <= signal32;
```

```
PCVAL <=signal32;
```

```
--signal1<=firstin;
```

```
end Behavioral;
```

**RTL**

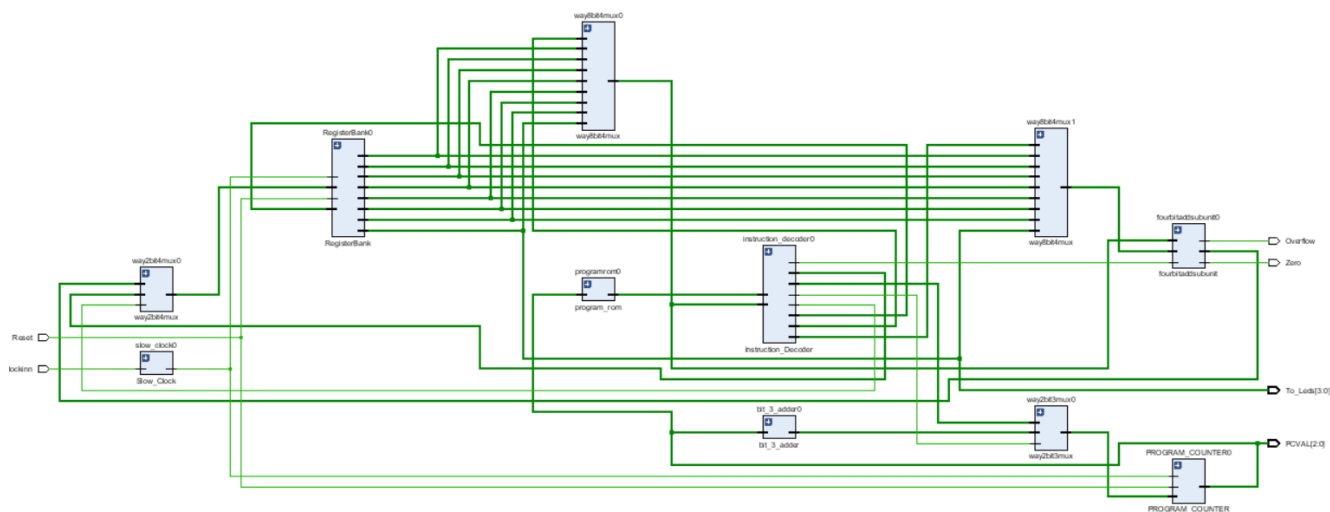

## Simulation Code

```

Zero=>Zero,
PCVAL=>PCVAL,
To_Leds=>To_Leds);

```

```

counte_process :process
begin
    clock <='0';
    wait for clk_period/2;
    clock <='1';
    wait for clk_period/2;
end process;

```

```

stiM_PROC :process
begin

    reset<='1';
    wait for 10ns;
    reset<='0';
    wait;

```


```

end process;
end;

```

\*\*\* When Simulation is done using **Slowclock** Some OUTPUT Values seems to be set to to "U"\*\*\*

## Behavioral Simulation

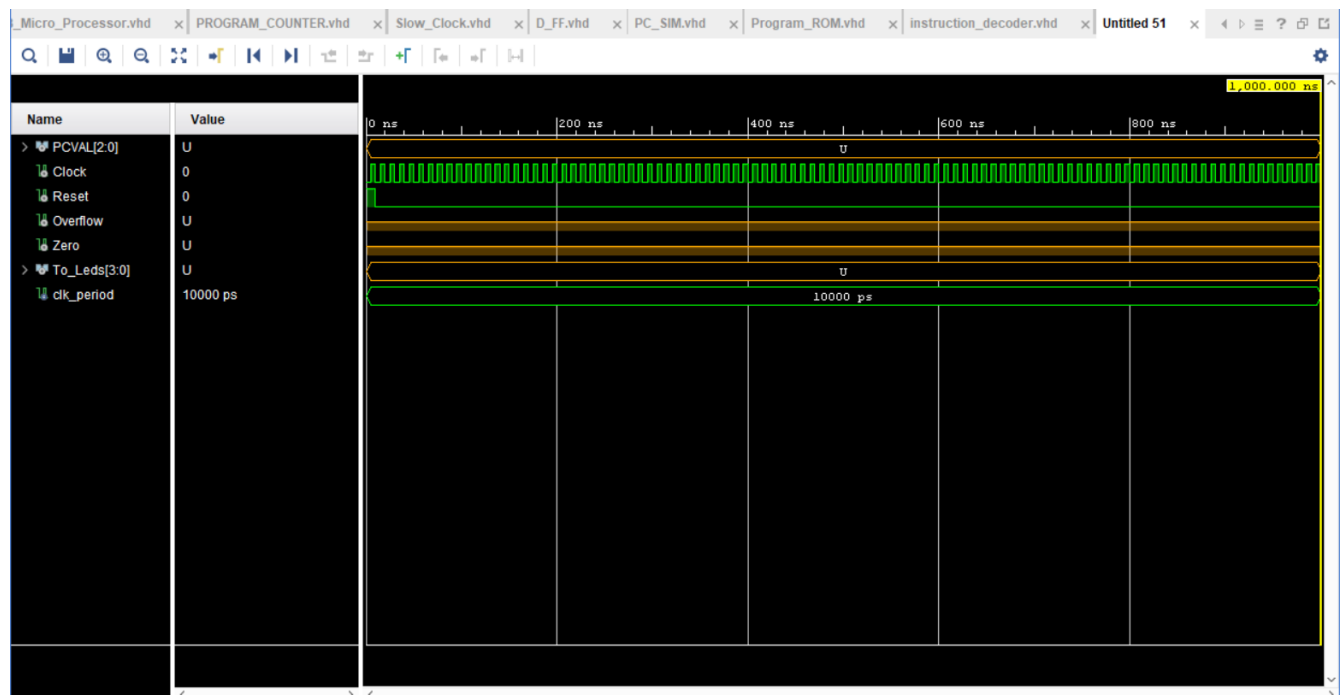



\*\*\* Hence for testing we use the processor without slow clock\*\*\*

## Code

```
entity Micro_Processor is
  Port ( Clockinn : in STD_LOGIC;
        Reset : in STD_LOGIC;
        Overflow : out STD_LOGIC;
        Zero : out STD_LOGIC;
        To_Leds : out STD_LOGIC_VECTOR (3 downto 0);
        PCVAL : out STD_LOGIC_VECTOR (2 downto 0));

end Micro_Processor;

architecture Behavioral of Micro_Processor is

  component PROGRAM_COUNTER
    Port ( TOIN : in STD_LOGIC_VECTOR (2 downto 0);
          TOOOUT : out STD_LOGIC_VECTOR (2 downto 0);
          CLK : in STD_LOGIC;
          RES : in STD_LOGIC);
  end component;

  component way2bit3mux
    Port ( jumpflag : in STD_LOGIC;
          addresstojump : in STD_LOGIC_VECTOR (2 downto 0);
          default1 : in STD_LOGIC_VECTOR (2 downto 0);
          out1 : out STD_LOGIC_VECTOR (2 downto 0));
  end component;

  component bit_3_adder
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
          S : out STD_LOGIC_VECTOR (2 downto 0)
        );
  end component;

  component program_rom is
    Port ( regsel : in STD_LOGIC_VECTOR (2 downto 0);
          out1 : out STD_LOGIC_VECTOR (11 downto 0));
  end component;

  component Instruction_Decoder is
    Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0);
          RegisterCheckkJump : in STD_LOGIC_VECTOR (3 downto 0);
          RegisterEnable : out STD_LOGIC_VECTOR (2 downto 0);
          LoadSelect : out STD_LOGIC;
          ImmValue : out STD_LOGIC_VECTOR (3 downto 0);
          RegisterSelect_1 : out STD_LOGIC_VECTOR (2 downto 0);
          RegisterSelect_2 : out STD_LOGIC_VECTOR (2 downto 0);
          AddSub_Select : out STD_LOGIC;
          JumpFlag : out STD_LOGIC;
          JumpAdder : out STD_LOGIC_VECTOR (2 downto 0));
```

end component;

component way2bit4mux is

```
Port ( loadsel : STD_LOGIC;  
      load : in STD_LOGIC_VECTOR (3 downto 0);  
      defaultval : in STD_LOGIC_VECTOR (3 downto 0);  
      outval : out STD_LOGIC_VECTOR (3 downto 0)  
    );
```

end component;

component Slow\_Clock is

```
Port ( Clk_in : in STD_LOGIC;  
      Clk_out : out STD_LOGIC);
```

end component;

component RegisterBank is

```
Port ( RegisterBank_In : in STD_LOGIC_VECTOR (3 downto 0) ;  
      RegisterBank_Reset : in STD_LOGIC;  
      Register_Select : in STD_LOGIC_VECTOR (2 downto 0);  
      Clock : in STD_LOGIC;  
      Register0_Out : out STD_LOGIC_VECTOR (3 downto 0);  
      Register1_Out : out STD_LOGIC_VECTOR (3 downto 0);  
      Register2_Out : out STD_LOGIC_VECTOR (3 downto 0);  
      Register3_Out : out STD_LOGIC_VECTOR (3 downto 0);  
      Register4_Out : out STD_LOGIC_VECTOR (3 downto 0);  
      Register5_Out : out STD_LOGIC_VECTOR (3 downto 0);  
      Register6_Out : out STD_LOGIC_VECTOR (3 downto 0);  
      Register7_Out : out STD_LOGIC_VECTOR (3 downto 0));
```

end component;

component way8bit4mux is

```
Port ( regsel : in STD_LOGIC_VECTOR (2 downto 0);  
      reg0 : in STD_LOGIC_VECTOR (3 downto 0);  
      reg1 : in STD_LOGIC_VECTOR (3 downto 0);  
      reg2 : in STD_LOGIC_VECTOR (3 downto 0);  
      reg3 : in STD_LOGIC_VECTOR (3 downto 0);  
      reg4 : in STD_LOGIC_VECTOR (3 downto 0);  
      reg5 : in STD_LOGIC_VECTOR (3 downto 0);  
      reg6 : in STD_LOGIC_VECTOR (3 downto 0);  
      reg7 : in STD_LOGIC_VECTOR (3 downto 0);  
      out1 : out STD_LOGIC_VECTOR (3 downto 0));
```

end component;

component fourbitaddsubunit is

```
Port ( A : in STD_LOGIC_VECTOR (3 downto 0);  
      B : in STD_LOGIC_VECTOR (3 downto 0);  
      Cal_Control : in STD_LOGIC;  
      Overflow : out STD_LOGIC;  
      Zero : out STD_LOGIC;  
      S : out STD_LOGIC_VECTOR (3 downto 0));
```

end component;

```

signal signal6,isolateclock,signalid2,signalid6,cclk,rres: STD_LOGIC;
signal signal1,signal2,signal3,signal4,signal5,signal32,signalid1,signalid4,signalid5 :
STD_LOGIC_VECTOR (2 downto 0);
signal signal7 : STD_LOGIC_VECTOR (11 downto 0);
signal signalid3,signal8,signal9,signalid7 : STD_LOGIC_VECTOR (3 downto 0);
signal rbout0,rbout1,rbout2,rbout3,rbout4,rbout5,rbout6,rbout7,signal10,signal11 :
STD_LOGIC_VECTOR (3 downto 0);

```

```

begin

```

```

PROGRAM_COUNTER0 : PROGRAM_COUNTER PORT MAP (

```

```

    TOIN =>signal1 ,
    TOOUT => signal32,
    CLK => cclk,
    res =>rres );

```

```

way2bit3mux0 : way2bit3mux Port map (

```

```

    jumpflag =>signal6,
    addresstojump =>signal5,
    default1 =>signal4,
    out1 =>signal11);

```

```

bit_3_adder0 : bit_3_adder Port map (

```

```

    A =>signal2,
    S =>signal4);

```

```

programrom0 : program_rom Port map (

```

```

    regsel =>signal3,
    out1 =>signal7 );

```

```

instruction_decoder0 : Instruction_Decoder Port map (

```

```

    Instruction =>signal7,
    RegisterCheckkJump =>signalid7,
    RegisterEnable =>signalid1,
    LoadSelect =>signalid2,
    ImmValue =>signalid3,
    RegisterSelect_1=>signalid4,
    RegisterSelect_2 =>signalid5,
    AddSub_Select =>signalid6,
    JumpFlag =>signal6,
    JumpAdder =>signal5);

```

```

way2bit4mux0 : way2bit4mux Port map (

```

```

    loadsel =>signalid2,
    load =>signalid3,
    defaultval =>signal9,
    outval =>signal8
);

```

```

slow_clock0 : Slow_Clock Port map (

```

```

    Clk_in =>isolateclock,

```

```
Clk_out=>isolateclock);
```


```
RegisterBank0 : RegisterBank Port map (  
    RegisterBank_In=>signal8,  
    RegisterBank_Reset =>rres,  
    Register_Select =>signalid1,  
    Clock =>cclk,  
    Register0_Out =>rbout0,  
    Register1_Out =>rbout1,  
    Register2_Out =>rbout2,  
    Register3_Out =>rbout3,  
    Register4_Out =>rbout4,  
    Register5_Out =>rbout5,  
    Register6_Out =>rbout6,  
    Register7_Out =>rbout7);
```

```
way8bit4mux0 : way8bit4mux Port map (  
    regsel =>signalid4,  
    reg0 =>rbout0,  
    reg1 =>rbout1,  
    reg2 =>rbout2,  
    reg3 =>rbout3,  
    reg4 =>rbout4,  
    reg5 =>rbout5,  
    reg6 =>rbout6,  
    reg7 =>rbout7,  
    out1 =>signal10);
```

```
way8bit4mux1 : way8bit4mux Port map (  
    regsel =>signalid5,  
    reg0 =>rbout0,  
    reg1 =>rbout1,  
    reg2 =>rbout2,  
    reg3 =>rbout3,  
    reg4 =>rbout4,  
    reg5 =>rbout5,  
    reg6 =>rbout6,  
    reg7 =>rbout7,  
    out1 =>signal11);
```

```
fourbitaddsubunit0 : fourbitaddsubunit Port map (  
    A =>signal10,  
    B =>signal11,  
    Cal_Control =>signalid6,  
    Overflow =>overflow,  
    Zero =>zero,  
    S =>signal9);
```

```
signalid7<=signal10;  
To_Leds(0)<=rbout7(0);  
To_Leds(1)<=rbout7(1);
```

 RTL

end component;

```

    signal PCVAL : STD_LOGIC_VECTOR (2 downto 0);
    signal Clock : STD_LOGIC;
    signal Reset : STD_LOGIC;
    signal Overflow : STD_LOGIC;
    signal Zero : STD_LOGIC;
    signal To_Leds : STD_LOGIC_VECTOR (3 downto 0);
    constant clk_period : time := 10 ns;

begin

    uut : Micro_Processor Port map (
        Clockinn=>Clock,
        Reset=>Reset,
        Overflow=>Overflow,
        Zero=>Zero,
        PCVAL=>PCVAL,
        To_Leds=>To_Leds);

    counte_process :process
    begin
        clock <='0';
        wait for clk_period/2;
        clock <='1';
        wait for clk_period/2;
    end process;

    stiM_PROC :process
    begin

        reset<='1';
        wait for 10ns;
        reset<='0';
        wait;

end process;
end;

```

### **Behavioral Simulation**

#### **:: TESTING 1 ::**

#### **ProgramROM**

```

signal ROM : rom_type :=(
    "101110000101",--- r7 <= 5


```

```

"101100000011",--- r6 <= 3
"011100000000",--- r6 <=-r6
"001111100000",--- r7 <= r7+r6
"100000000000",-- r0<=0
"100000000000",--- r0<=0
"100000000000",--- r0<=0
"100000000000" --- r0<=0
);

```

## **OUTPUT**

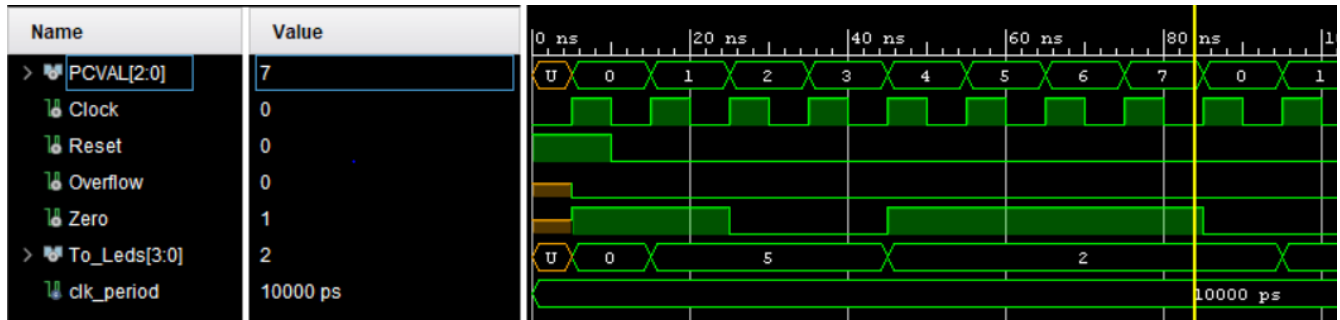

## **:: TESTING 2 ::**

### **ProgramROM**

```

signal ROM : rom_type :=(
    "101110000101",--- r7 <= 5
    "101100000011",--- r6 <= 3
    "011100000000",--- r6 <=-r6
    "001111100000",--- r7 <= r7+r6
    "100000000000",-- r0<=0
    "100000000000",--- r0<=0
    "100000000000",--- r0<=0
    "100000000000" --- r0<=0
);

```


### **TB\_CODE**

```

reset<='1';
wait for 10ns;
reset<='0';
wait for 20ns;
reset<='1';
wait for 10ns;
reset<='0';
wait;

```

## **OUTPUT**

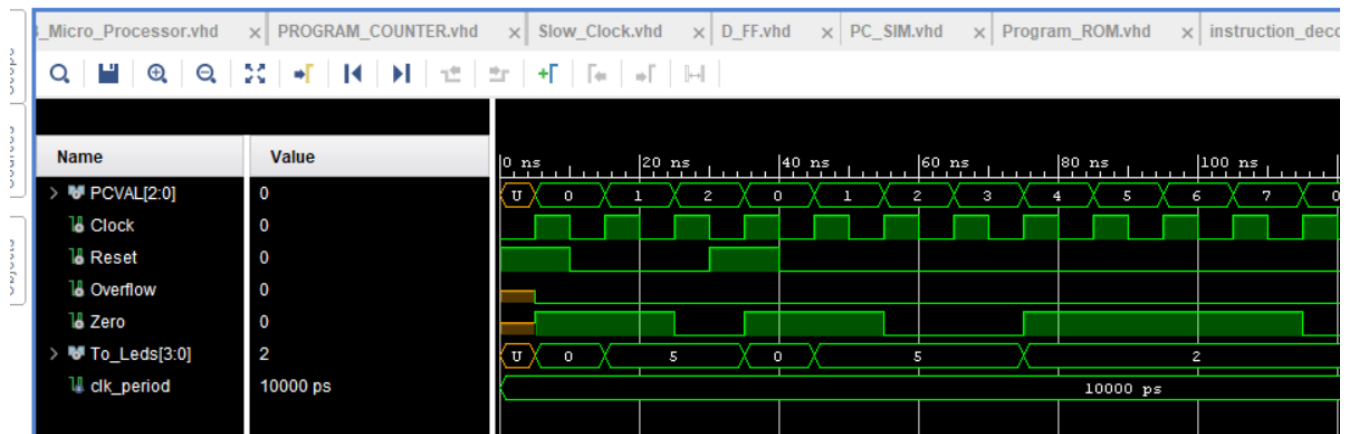

## :: TESTING 3 ::

### ProgramROM

```

signal ROM : rom_type :=(
    "101110000000",--- r7 <= 0
    "101000000010",--- r4 <= 2
    "101100000011",--- r6 <= 3
    "101010000001",--- r5 <= 1
    "011010000000",--- r5 <= -r5
    "001111000000",--- r7 <= r7+r4
    "001101010000",--- r6 <= r6+r5
    "111100000101" --- PC <= 5
);

```

### TB\_CODE

```

reset<='1';
wait for 10ns;
reset<='0';

```

### OUTPUT



